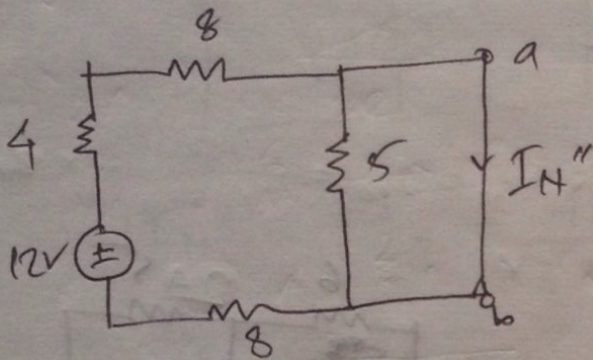


Current won't flow through 5Ω .

$$\downarrow I_{N'} = \frac{4 \times 2}{8+8+4} = 0.4 \text{ A}$$

When 12V is active




Current won't flow through 5Ω

$$R_{eq} = 4 + 8 + 8 = 20 \Omega$$



$$\therefore I = \frac{V}{R_{eq}} = \frac{12}{20} = 0.6 \text{ A}$$

$$\therefore \downarrow I_{N''} = I = 0.6 \text{ A}$$
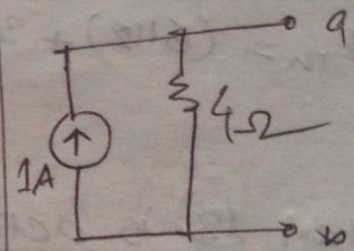
$$\begin{aligned} \therefore I_H &= \downarrow I_{N'} + \downarrow I_{N''} \\ &= 0.4 + 0.6 = 1 \text{ A} \end{aligned}$$




Ex-4.13

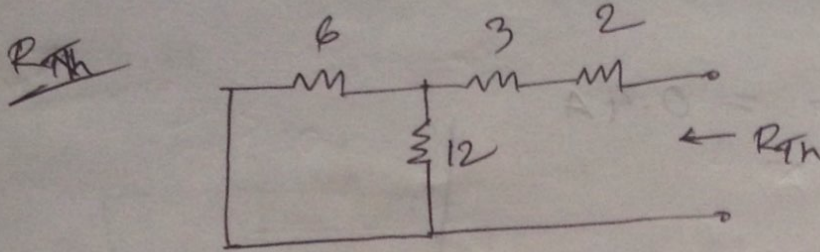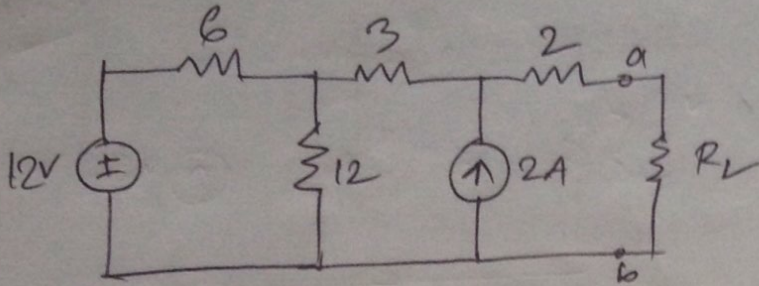

$$R_{Th} = (6 \parallel 12) + 3 + 2 = 9 \Omega$$

V_{Th}
when 12 is active.

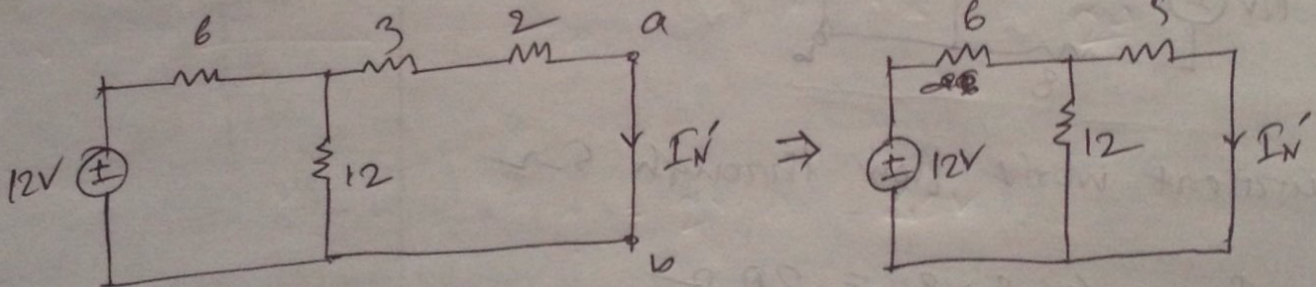

$$\therefore I = \frac{V}{R_{eq}} = \frac{12}{9.53} = 1.26 A$$

$\begin{pmatrix} 34 \\ 29 \end{pmatrix}$


$$R_{eq} = (5 \parallel 12) + 6 = 9.53 \Omega$$

$\begin{pmatrix} 162 \\ 17 \end{pmatrix}$

$$\therefore \downarrow I_{N'} = I_{5\Omega} = \frac{12 \times 1.26}{12 + 5} = 0.89 A$$


$\begin{pmatrix} 81 \\ 9 \end{pmatrix}$

When 2A is active

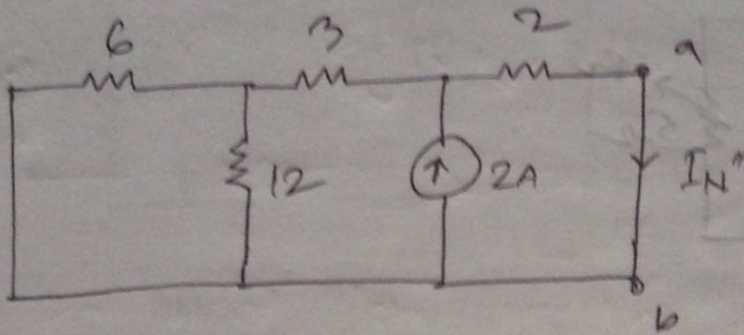

$$(12 || 6) + 3 = 4 \Omega$$

The circuit can be ~~be~~ reduced to -

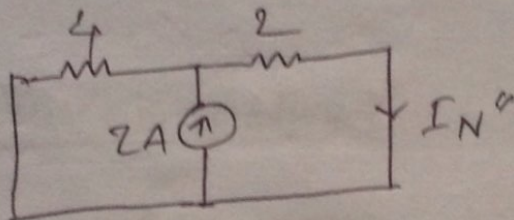


$$\therefore \downarrow I_N'' = I_{2\Omega} = \frac{4 \times 2}{4 + 2} = 1.33 \text{ A} \quad \left(\frac{4}{3} \right)$$

$$\therefore I_N = \downarrow I_N' + \downarrow I_N'' = 0.89 + 1.33 = 2.22 \text{ A} \quad \left(\frac{20}{9} \right)$$


$$\therefore V_{Th} = I_N R_{Th} = 2.22 \times 9 = 19.98 \text{ V} \approx 20 \text{ V}$$

Exercise

4.33

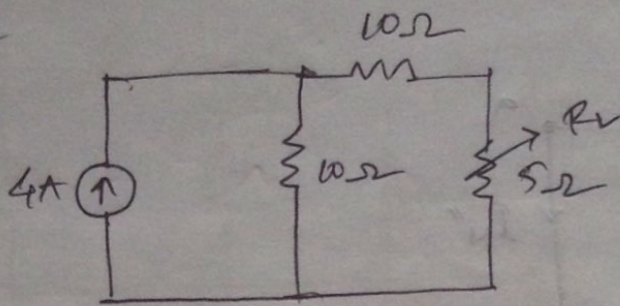


R_{Th}

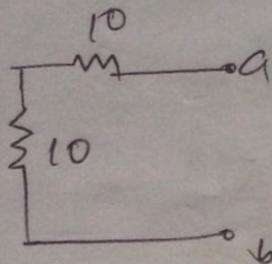


$$R_{Th} = 10 + 10 = 20\Omega$$

V_{Th}


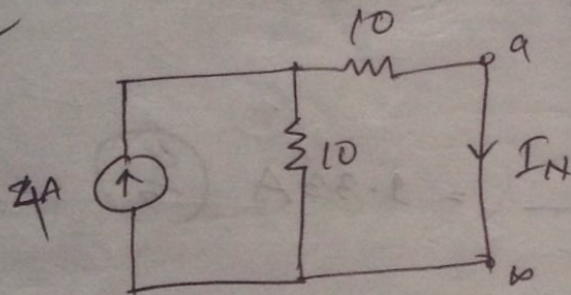


$$I_N = I_{10} = \frac{10}{10+10} \times 4 = 2A$$

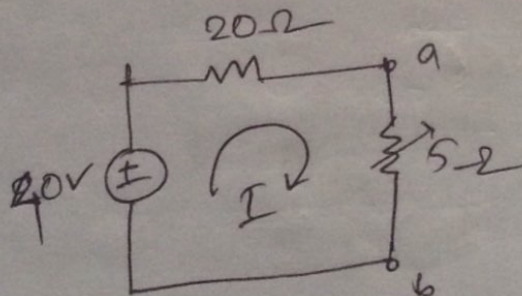
$$\therefore V_{Th} = I_N R_{Th} = 2 \times 20 = 40V$$


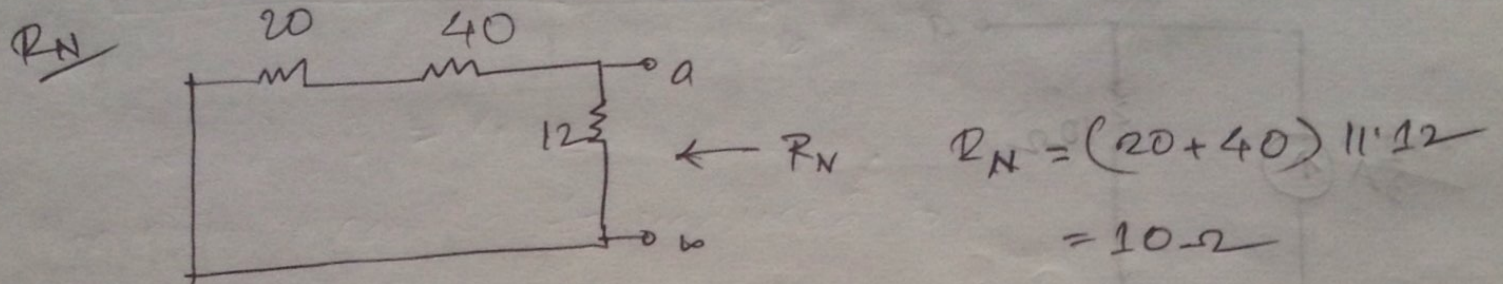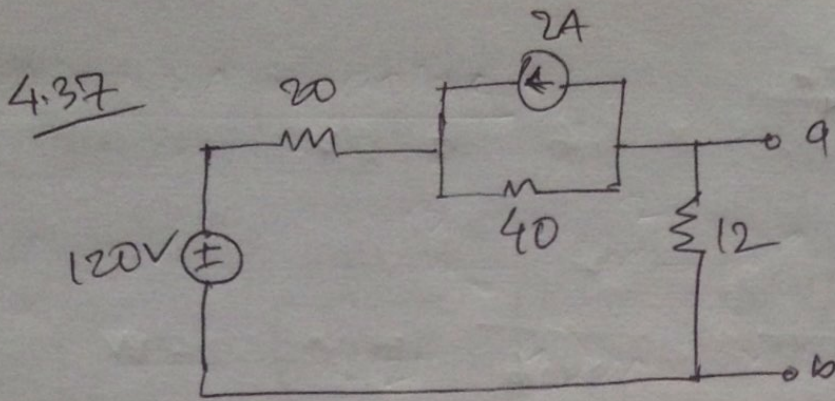
$$I_{5\Omega} = I = \frac{40}{20+5} = 1.6A$$




I_N when 120V is active

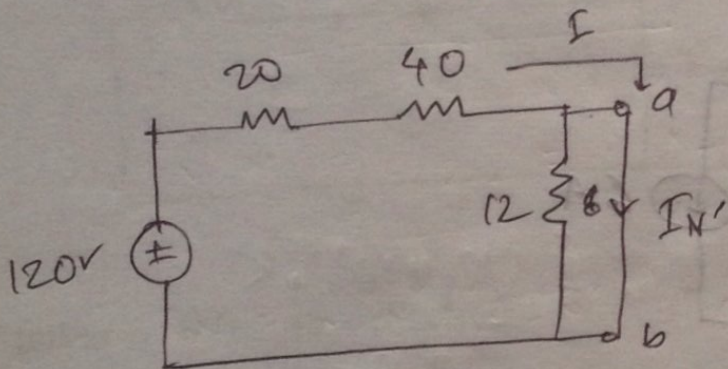

Current won't flow through 12Ω

$$\downarrow I_N' = I = \frac{120}{20 + 40} = 2A$$


when 2A is active

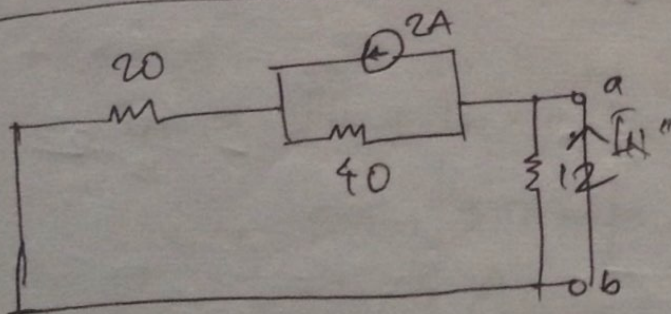


current won't flow through 12Ω .

$$\uparrow I_N'' = I_{20\Omega} = \frac{40 \times 2}{40 + 20} = \frac{4}{3} A$$

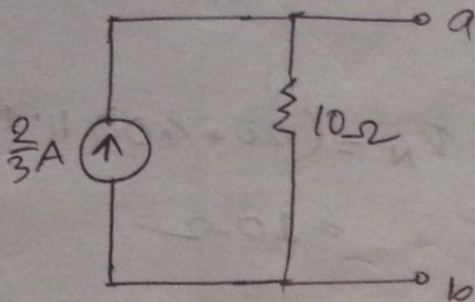
$$\begin{aligned}
 \therefore \downarrow I_N &= \downarrow I_{N'} - \uparrow I_{N''} \\
 &= 2 - \frac{4}{3} \\
 &= \frac{2}{3} \text{ A}
 \end{aligned}$$



4.66

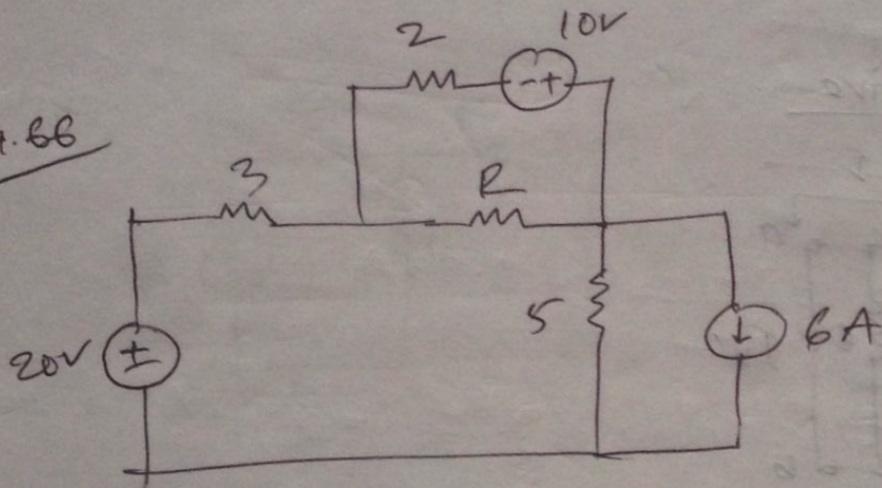


R_{Th}

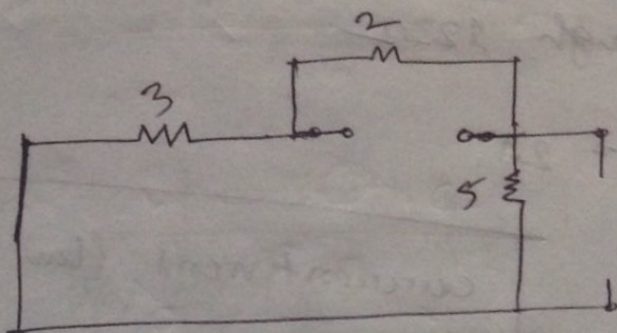

$$\begin{aligned}
 R_{Th} &= (5+3) \parallel 2 \\
 &= 1.6 \Omega
 \end{aligned}$$

I_N

When 20V is active

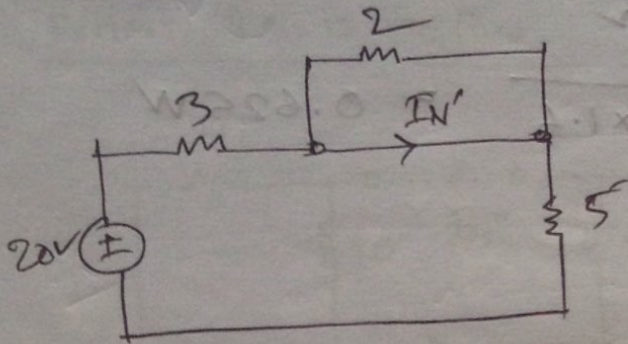


Current won't flow through

2-2

$$\therefore \vec{I}_{N'} = I = \frac{20}{3+5} = 2.5A$$


When 10V is active

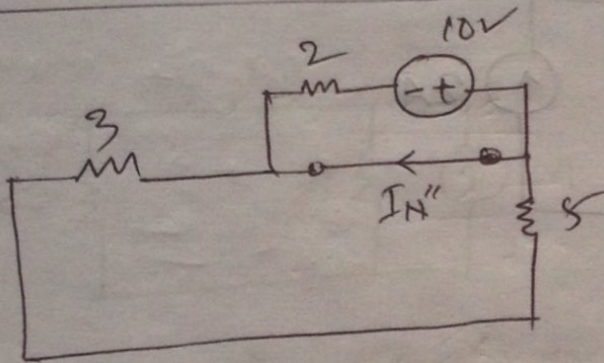

Current won't flow through
5-2 and 3-2.

$$\therefore \vec{I}_{N''} = \frac{10}{2} = 5A$$

When 6A is active

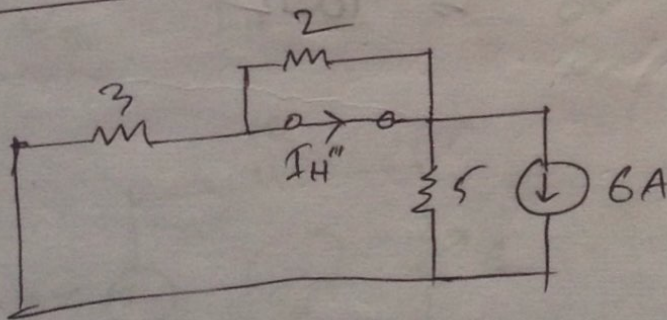

Current won't flow
through 2-2.


$$\therefore \vec{I}_{N'''} = I_{3\Omega} = \frac{5 \times 6}{3+5} = 3.75A$$

$$\begin{aligned} \therefore I_N &= \vec{I}_{N'} + \vec{I}_{N'''} - \vec{I}_{N''} \\ &= 2.5 + 3.75 - 5 \\ \therefore \vec{I}_N &= 1.25A \end{aligned}$$


$$\therefore V_{Th} = I_H R_{Th} = 1.25 \times 1.6 = 2V$$

$$P_{max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{2^2}{4 \times 1.6} = 0.625W$$

4.43

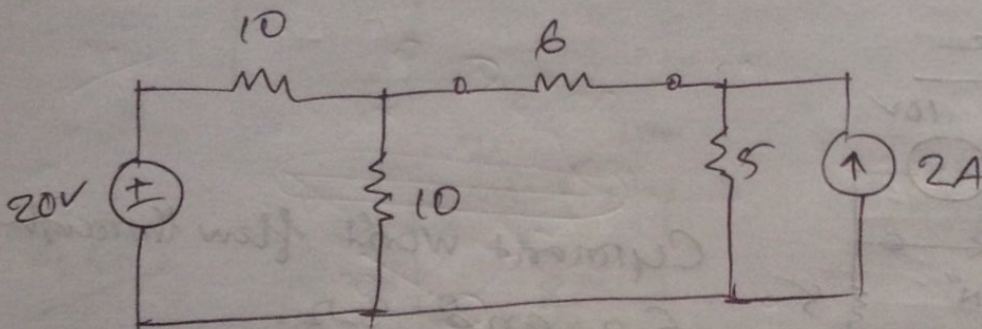


R_{Th}

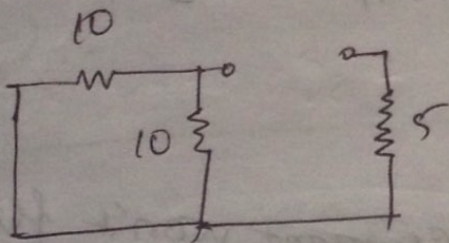

$$R_{Th} = (10 \parallel 10) + 5 = 10 \Omega$$

V_{Th}

When 20V is active

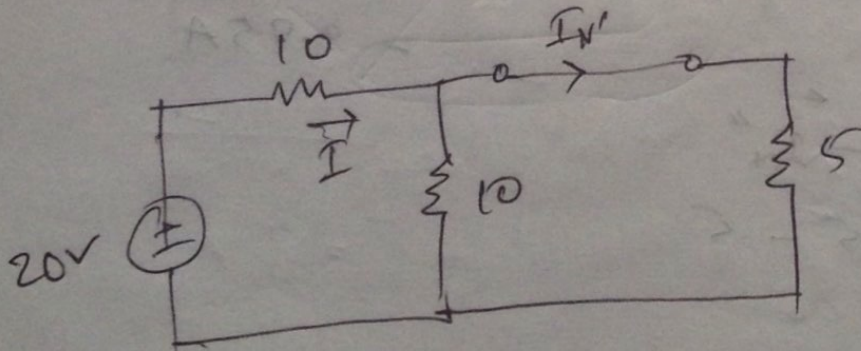


$$R_{eq} = (10 \parallel 5) + 10 = \frac{40}{3} \Omega$$


$$\therefore I = \frac{20}{\frac{40}{3}} = 1.5A$$

$$\therefore \vec{I_H'} = I_{5-2} = \frac{10 \times 1.5}{10+5} = 1A$$

When 2A is active

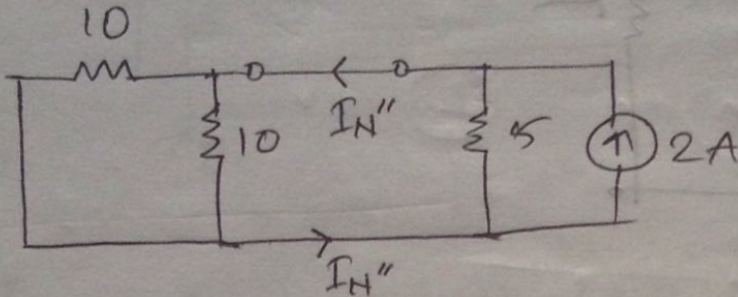


$$10 \parallel 10 = 5 \Omega$$

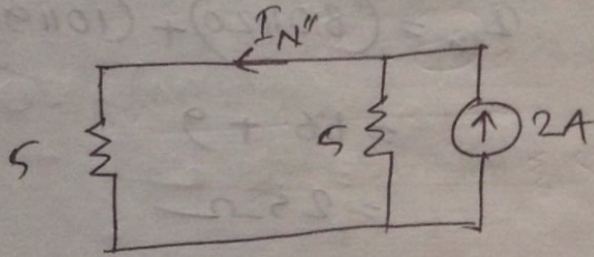

$$I_H'' = \frac{5 \times 2}{5+5} = 1A$$

$$\therefore I_H = \vec{I_H'} - \vec{I_H''} = 1 - 1 = 0A$$


$$\therefore V_{th} = I_H R_{th} = 0V$$

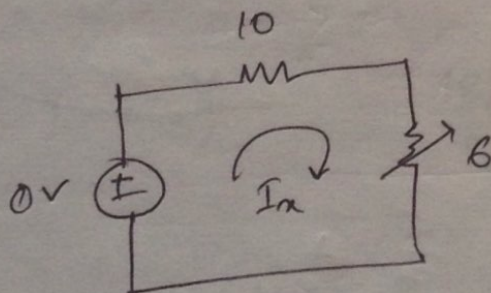


$$I_x = \frac{0}{10+6} = 0A$$

AUT-15

3b

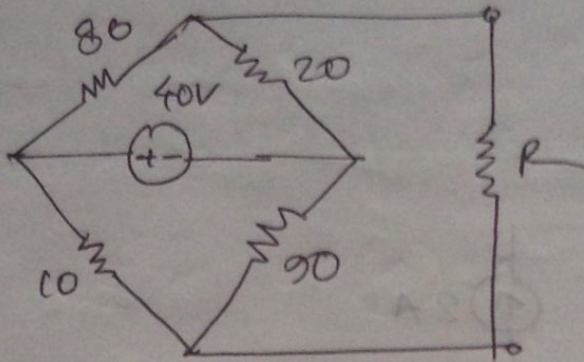


R_{th}

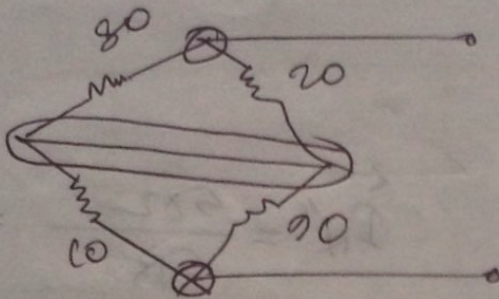


$$\begin{aligned} R_{th} &= (80 \parallel 20) + (10 \parallel 90) \\ &= 16 + 9 \\ &= 25 \Omega \end{aligned}$$

R must be 25Ω for maximum power.

V_{th}

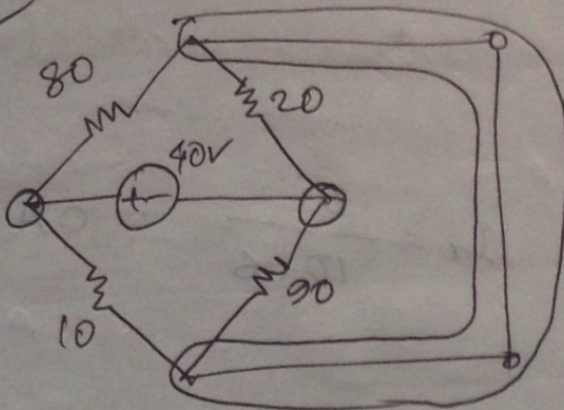

7b

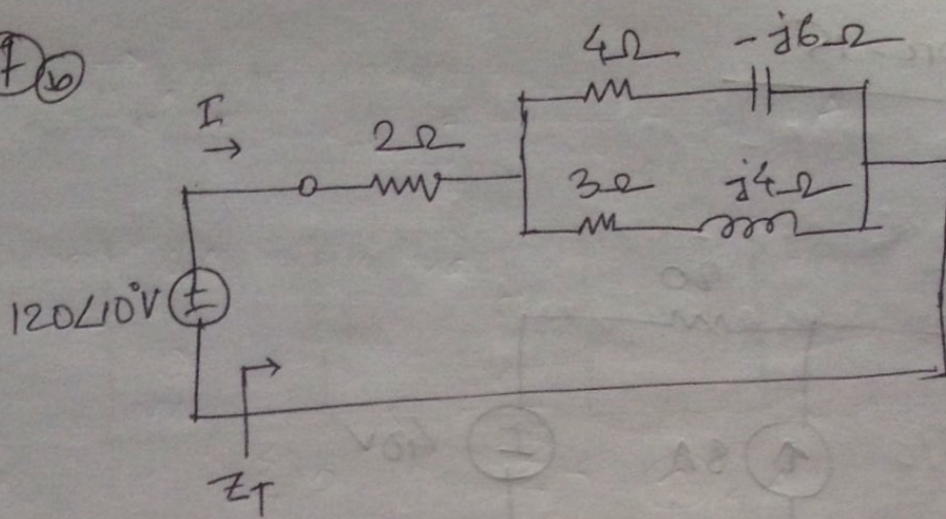

$$Z_T = 2 + \left\{ (4 - j6) \parallel (3 + j4) \right\}$$

$$= 2 + \frac{(4 - j6)(3 + j4)}{4 - j6 + 3 + j4}$$

$$= 2 + \frac{36 - 2j}{7 - j2}$$

$$= 2 + 4.83 + j1.09$$


$$\therefore Z_T = 6.83 + j1.09$$

$$= 6.92 \angle 9.1^\circ$$


$$\therefore I = \frac{V}{Z_T} = \frac{120 \angle 10^\circ}{6.92 \angle 9.1^\circ} = 17.35 \angle 0.9^\circ \quad (\text{Ans})$$

6pr-15

36

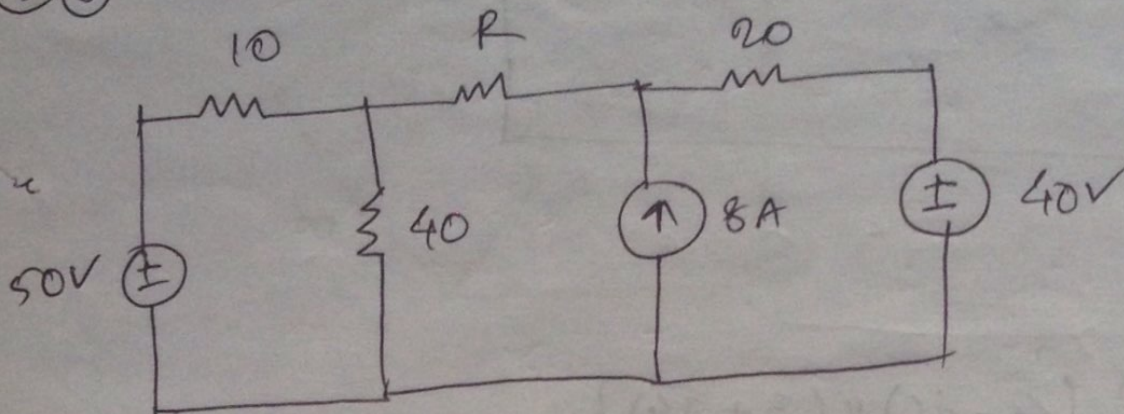


R_{th}

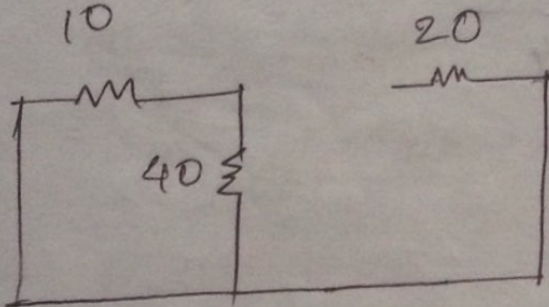

$$R_{th} = (10 \parallel 40) + 20 \\ = 28 \Omega$$

V_{th}

When 50V is active

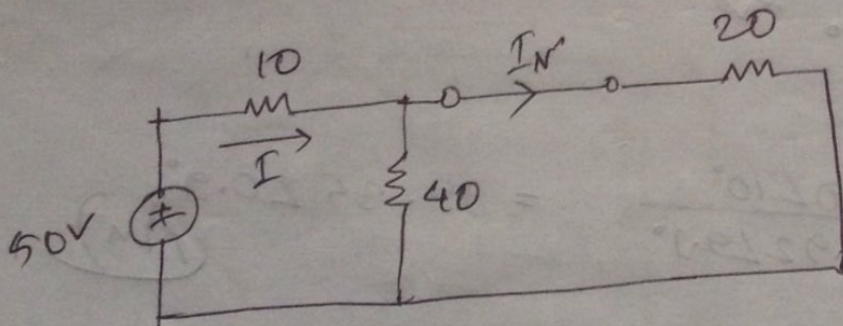


$$R_{eq} = (20 \parallel 40) + 10 \\ = \frac{70}{3}$$


$$\therefore I = \frac{50}{\frac{70}{3}} = \frac{15}{7} \text{ A}$$

$$\therefore I_{N'} = I_{20\Omega} = \frac{40 \times \frac{15}{7}}{40 + 20} = \frac{10}{7} \text{ A}$$

When 8A is active

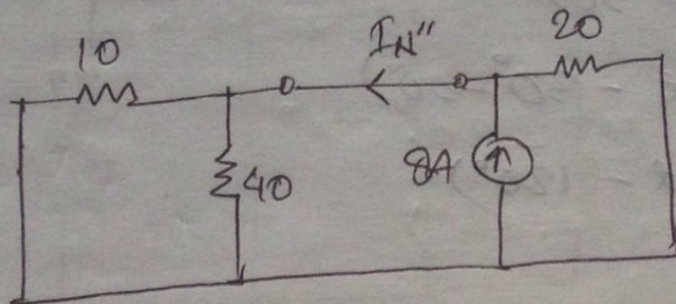


$$10 \parallel 40 = 8 \Omega$$

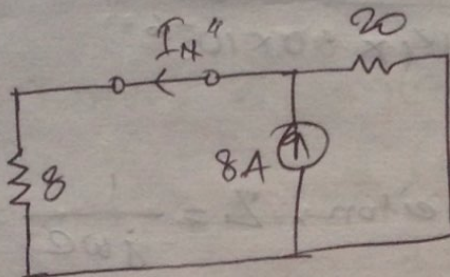

$$\therefore I_N'' = \frac{20 \times 8}{20 + 8} = \frac{40}{7} \text{ A}$$

When 40V is active

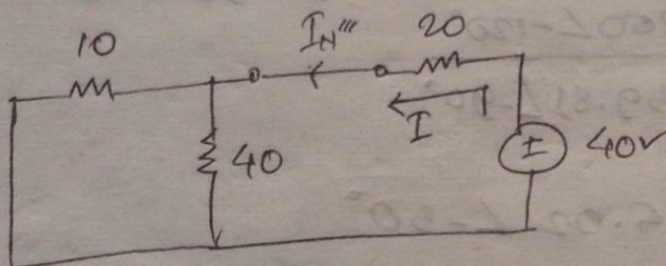

$$R_{eq} = (10 \parallel 40) + 20 = 28 \Omega$$

$$\therefore I = \frac{40}{28} = \frac{10}{7} \text{ A}$$

$$\therefore I_N''' = I = \frac{10}{7} \text{ A}$$

$$\begin{aligned} \therefore I_N &= I_N'' + I_N''' - I_N' \\ &= \frac{10}{7} + \frac{40}{7} - \frac{10}{7} \end{aligned}$$

$$\therefore I_N = \frac{40}{7} \text{ A}$$

$$\begin{aligned} \therefore V_{Th} &= I_N \times R_{Th} \\ &= \frac{40}{7} \times 28 \\ &= 160 \text{ V} \end{aligned}$$

$$P_{max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{228.57 \text{ V}}{57 \text{ V}}$$

Ans.