

By show that $V = j\omega L I$.

For an inductor, let us assume that the current through it,

$$i = I_m \cos(\omega t + \phi)$$

The voltage across it,

$$\begin{aligned} V &= L \frac{di}{dt} \\ &= L \frac{d}{dt} I_m \cos(\omega t + \phi) \\ &= -\omega L I_m \sin(\omega t + \phi) \\ &= \omega L I_m \cos(\omega t + \phi + 90^\circ) \\ &= \operatorname{Re}(\omega L I_m e^{j(\omega t + \phi + 90^\circ)}) \end{aligned}$$

Transforming into phasor,

$$\begin{aligned} V &= \omega L I_m e^{j(\phi + 90^\circ)} \\ &= \omega L I_m \cdot e^{j\phi} \cdot e^{j90^\circ} \\ &= j\omega L I_m e^{j\phi} [\because e^{j90^\circ} = j] \\ \Rightarrow V &= j\omega L I \quad [\because I_m e^{j\phi} = I_m \angle \phi = I] \end{aligned}$$

We can see that the current lags the voltage by 90° .

Draw the Phasor relationship for circuit elements :
capacitor and Inductor.

For a capacitor,

$$V = V_m \cos(\omega t + \phi)$$

$$i = I_m \cos(\omega t + \phi + 90^\circ)$$

So, current leads the voltage by 90° .

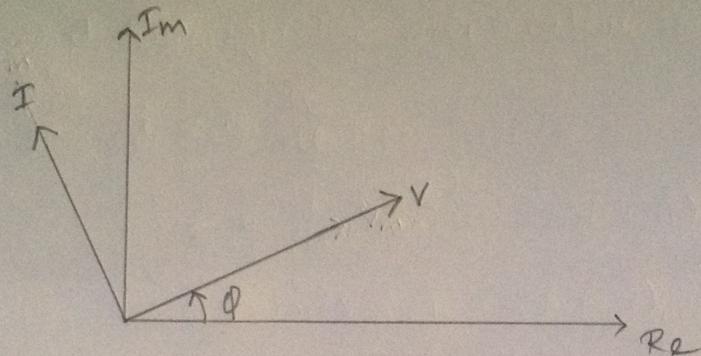


Figure : Phasor diagram for Capacitor .

For an inductor,

$$i = I_m \cos(\omega t + \phi)$$

$$V = V_m \cos(\omega t + \phi - 90^\circ)$$

so, voltage leads the current by 90°


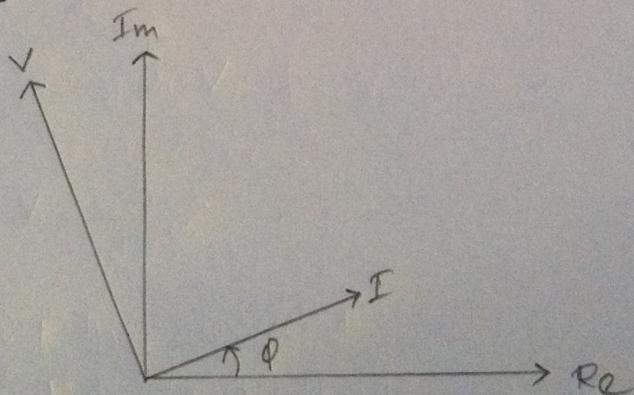



Figure : Phasor diagram for Inductor .
Name : Mahmood / 1AM / C161026

CIRCUIT PROBLEMS

Prac - 4.8

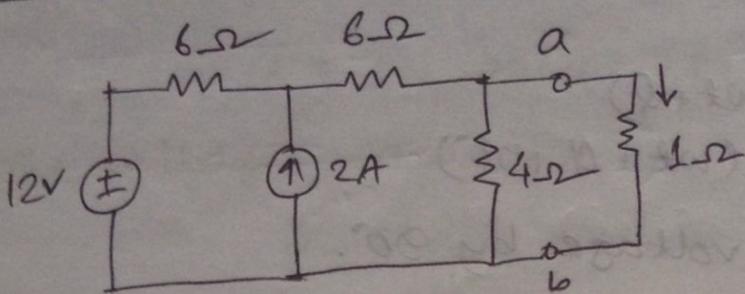


For obtaining R_{Th} ,

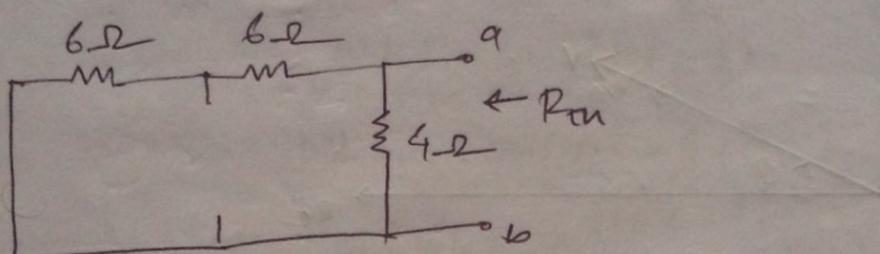


$$R_{Th} = (6+6) \parallel 4 = 3\Omega$$


For obtaining V_{Th} ,

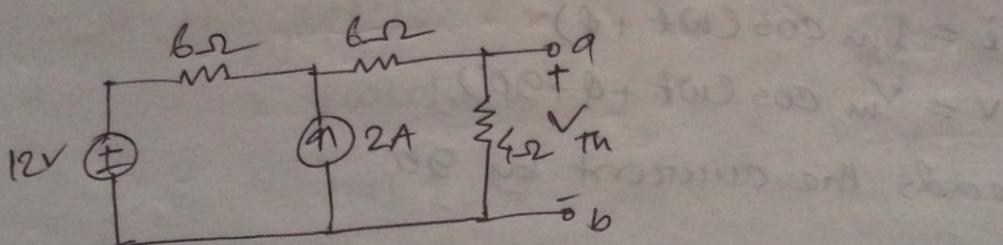

We will use Norton analysis

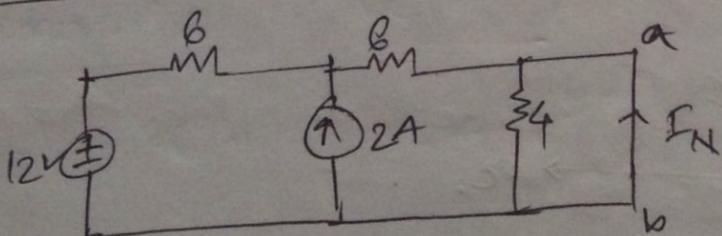

When 12V is active,

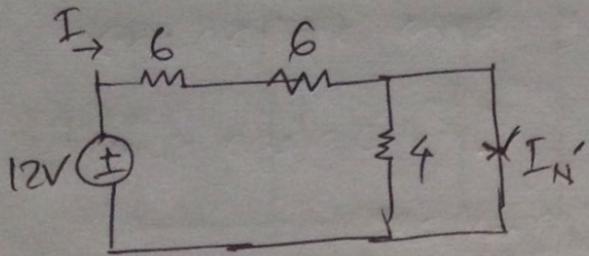


Current won't flow through 4Ω as there is a short circuit across it.

$$R' = 6 + 6 = 12$$

$$\therefore I = \frac{V}{R} = \frac{12}{12} = 1A$$

$$\text{So, } \downarrow I_{N'} = I = 1A$$

When 2A is active,

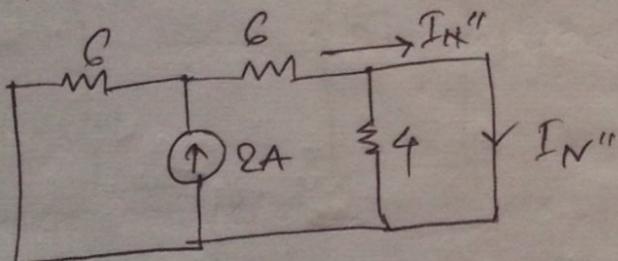


Current won't flow through 4Ω .

$$\therefore \downarrow I_{N''} = \frac{6}{6+6} \times 2$$

$$= 1A$$


$$\therefore I_H = I_{N'} + I_{N''} = 1A + 1A = 2A$$
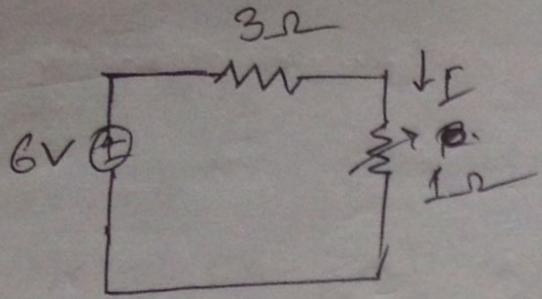
$$\begin{aligned}\therefore V_{Th} &= I_H R_{Th} \\ &= 2 \times 3 \\ &= 6V\end{aligned}$$




$$\therefore I = \frac{6}{3+1} = 1.5A$$

Prob 4.11

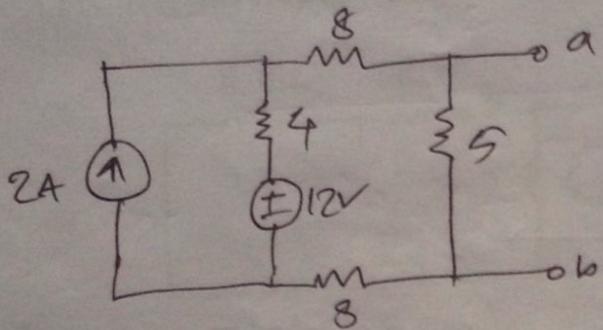


R_N

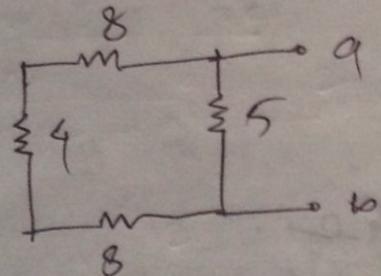

$$R_N = (8+4+8) \parallel 5 \\ = 4\Omega$$



I_N
when 2A is active

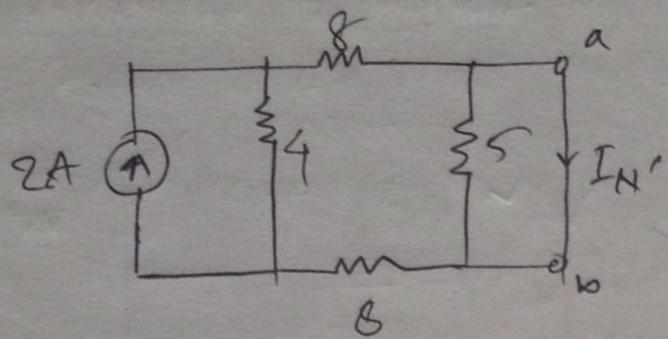

Current won't flow through S_{22} .

$$\downarrow I_{N'} = \frac{4 \times 2}{8+8+4} = 0.4 \text{ A}$$

when 12V is active

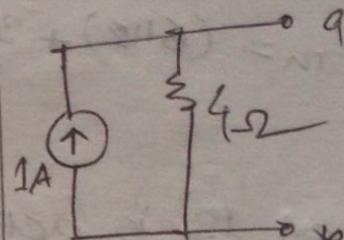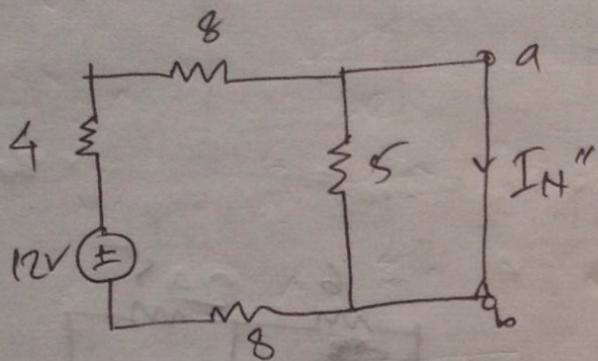

Current won't flow through S_{22}



$$R_{eq} = 4 + 8 + 8 = 20 \Omega$$

$$\therefore I = \frac{V}{R_{eq}} = \frac{12}{20} = 0.6 \text{ A}$$

$$\therefore \downarrow I_{N''} = I = 0.6 \text{ A}$$

$$\begin{aligned} \therefore I_H^* &= \downarrow I_{H'} + \downarrow I_{H''} \\ &= 0.4 + 0.6 = 1 \text{ A} \end{aligned}$$



Ex-4.13

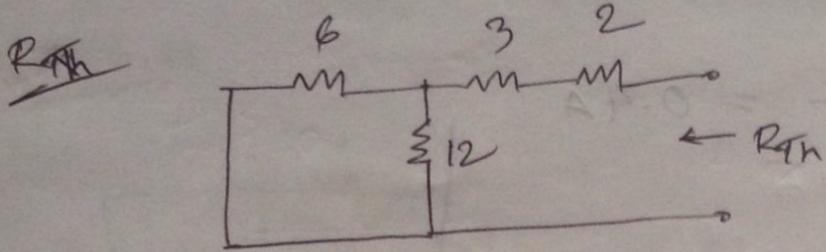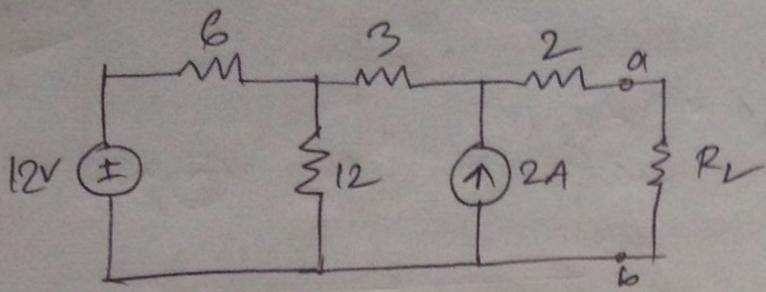

$$R_{Th} = (6 \parallel 12) + 3 + 2 = 9 \Omega$$

V_{Th}

when 12 is active.

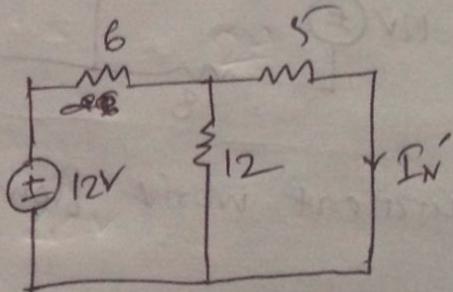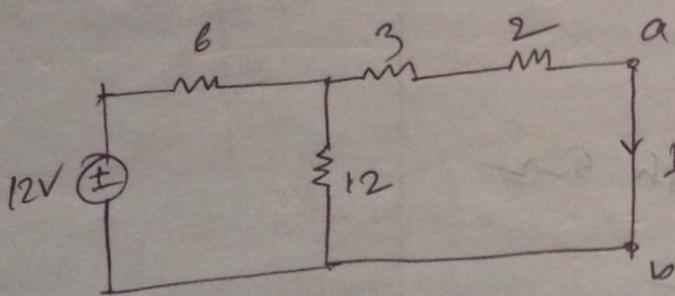

$$\therefore I = \frac{V}{R_{eq}} = \frac{12}{9.53} = 1.26 A$$


$$R_{eq} = (5 \parallel 12) + 6 = 9.53 \Omega$$

$$\frac{162}{17}$$

$$\therefore I_{N'} = I_{5\Omega} = \frac{12 \times 1.26}{12+5} = 0.89 A$$


$$\frac{8}{9}$$

When 2A is active

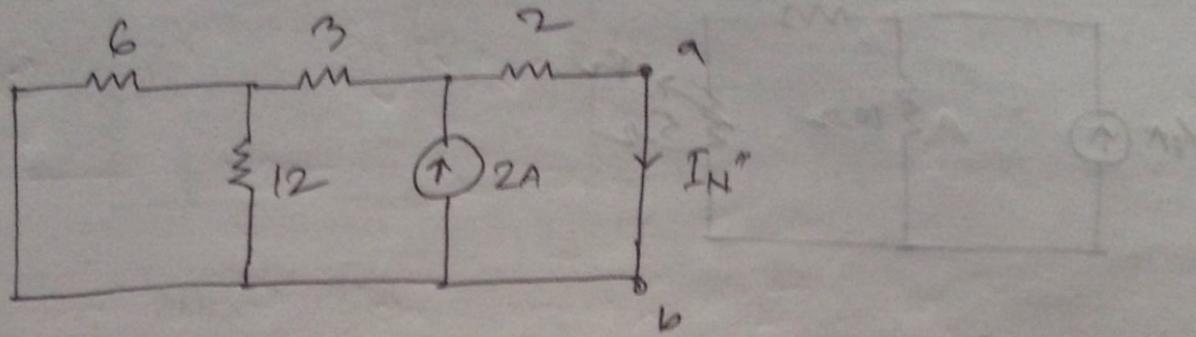

$$(12 \parallel 6) + 3 = 4 \Omega$$

The circuit can be reduced to -

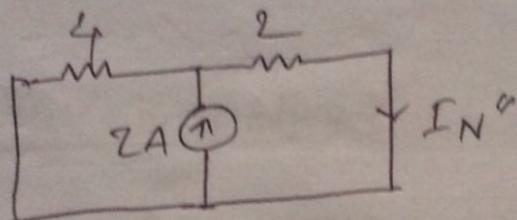



$$\therefore I_{N''} = I_{2,2} = \frac{4 \times 2}{4+2} = 1.33A \quad \left(\frac{4}{3}\right)$$

$$\therefore I_N = I_{N'} + I_{N''} = 0.89 + 1.33 = 2.22A \quad \left(\frac{20}{9}\right)$$


$$\therefore V_{Th} = I_N R_{Th} = 2.22 \times 9 = 19.98V \approx 20V$$

Exercise

4.33

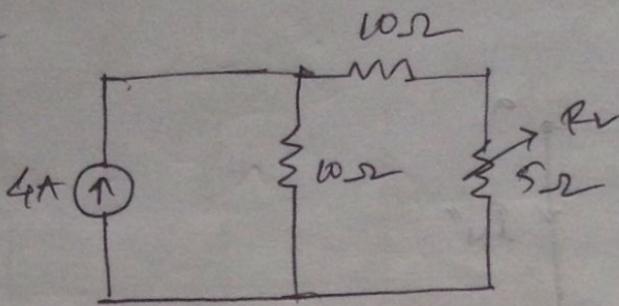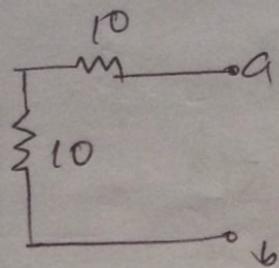
R_{Th}

$$R_{Th} = 10 + 10 = 20\Omega$$

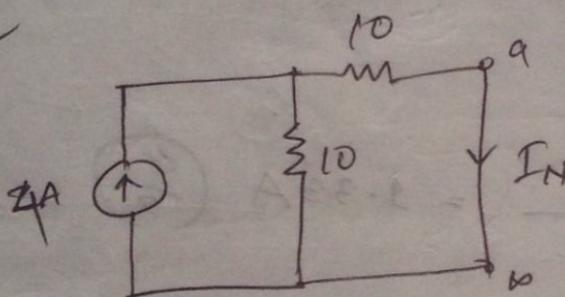V_{Th}


$$\begin{aligned} \uparrow I_H &= I_{10} = \frac{10}{10+10} \times 4 \\ &= 2A \end{aligned}$$
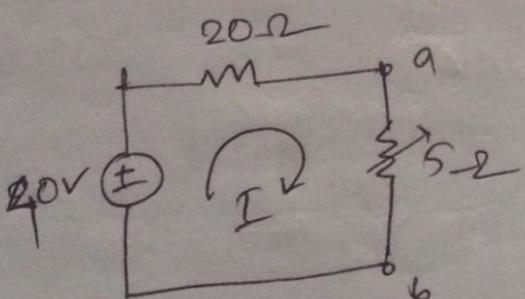
$$\therefore V_{Th} = I_N R_{Th} = 2 \times 20 = 20V$$




$$I_{5\Omega} = I = \frac{20}{20+5} = \cancel{0.8A} \quad 1.6A$$

4.37

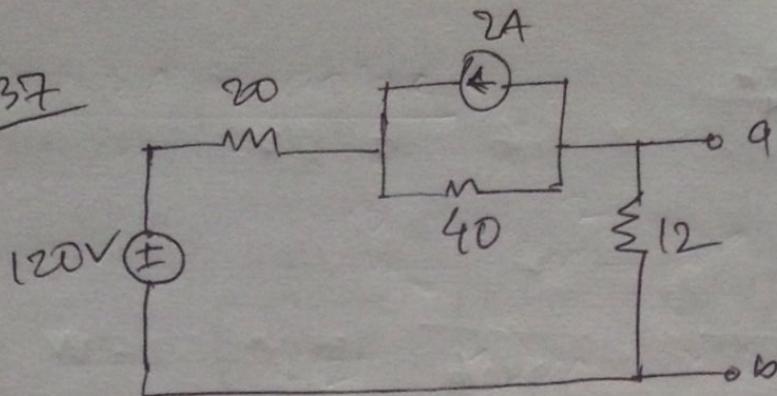


R_N

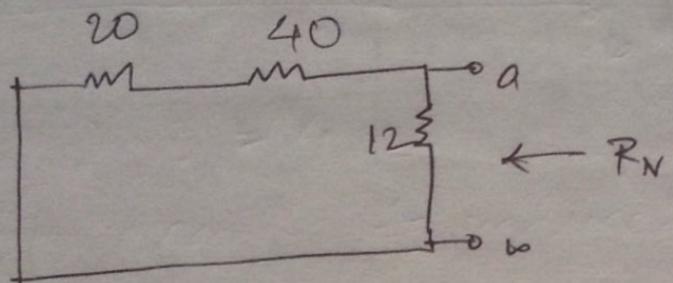

$$R_N = (20 + 40) \parallel 12 = 10 \Omega$$


When 120V is active

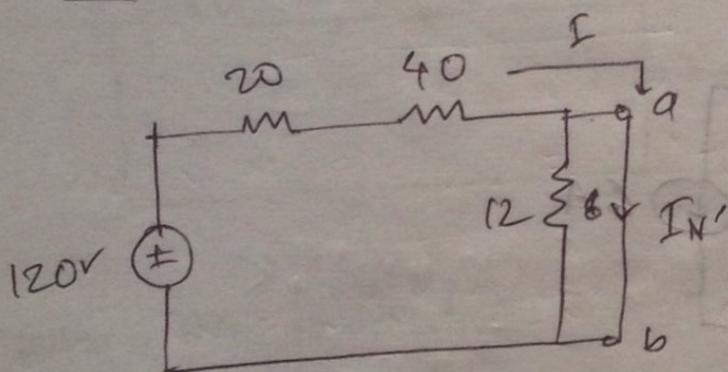

current won't flow through 12Ω

$$\downarrow I_{N'} = I = \frac{120}{20+40} = 2A$$

When 2A is active

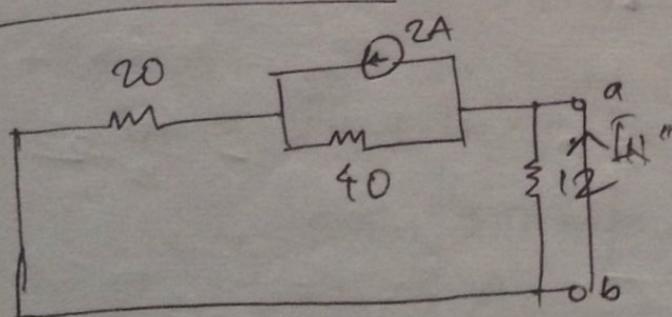




current won't flow through 12Ω .

$$\uparrow I_{N''} = I_{20\Omega} = \frac{40 \times 2}{40+20} = \frac{4}{3} A$$

$$\therefore \downarrow I_N = \downarrow I_{N'} - \uparrow I_{N''}$$

$$= 2 - \frac{4}{3}$$

$$= \frac{2}{3} A$$

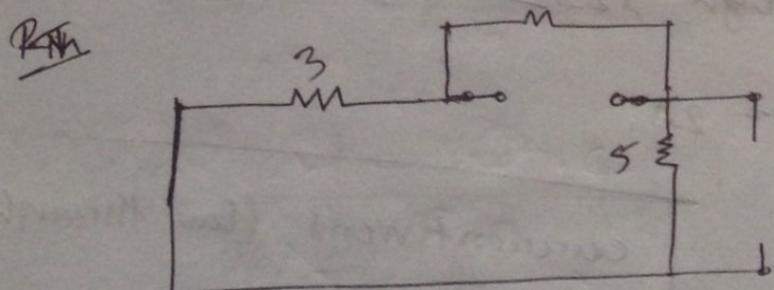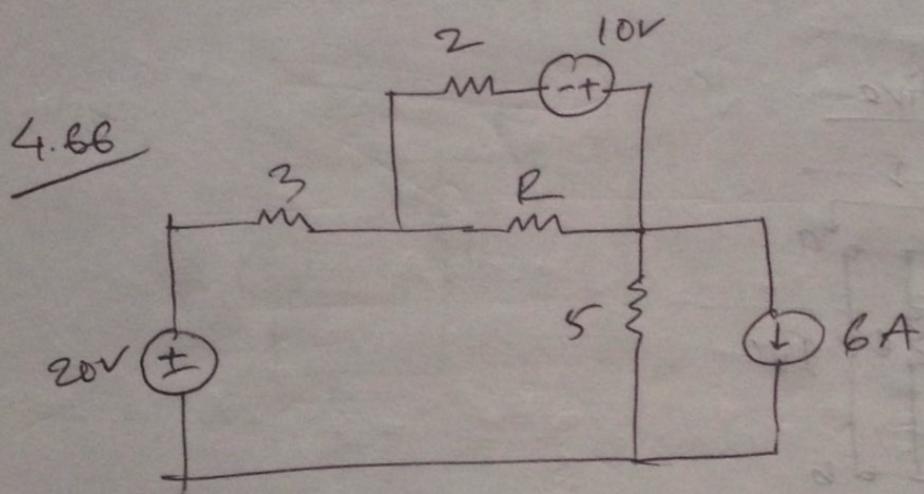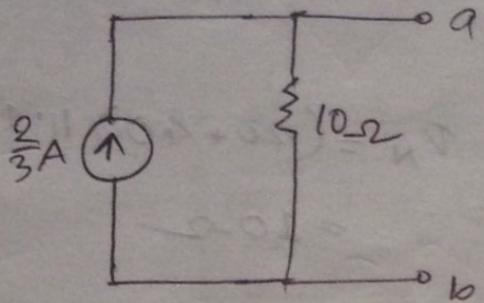


$$R_{th} = (5+3) \parallel 2$$

$$= 1.6 \Omega$$

I_N

When 20V is active

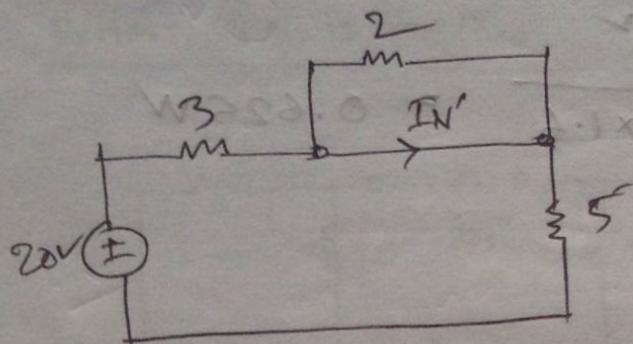


current won't flow through

2Ω

$$\therefore \vec{I}_{N'} = I = \frac{20}{3+5} = 2.5A$$


When 10V is active

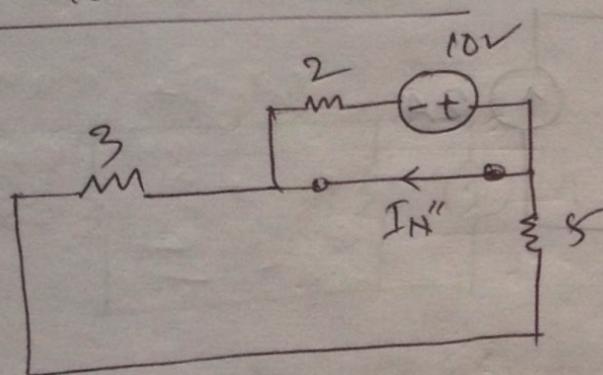

current won't flow through
5Ω and 3Ω.

$$\therefore \vec{I}_{N''} = \frac{10}{2} = 5A$$

When 6A is active

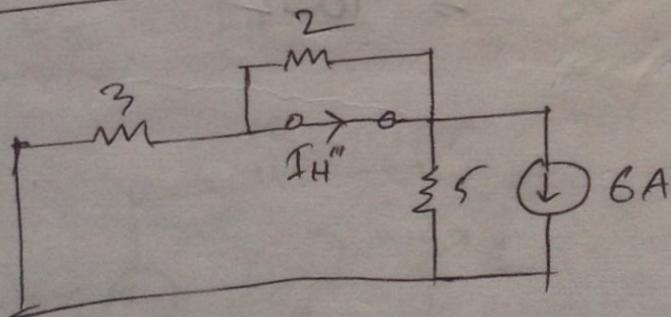

current won't flow
through 2Ω.

$$\therefore \vec{I}_{N'''} = I_{2\Omega} = \frac{5 \times 6}{3+5}$$

$$= 3.75A$$

$$\therefore \vec{I}_N = \vec{I}_{N'} + \vec{I}_{N''} - \vec{I}_{N'''}$$


$$= 2.5 + 3.75 - 5$$

$$\therefore \vec{I}_N = 1.25A$$


$$\therefore V_{Th} = I_H R_{Th} = 1.25 \times 1.6 = 2V$$

$$P_{max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{2^2}{4 \times 1.6} = 0.625W$$

4.43

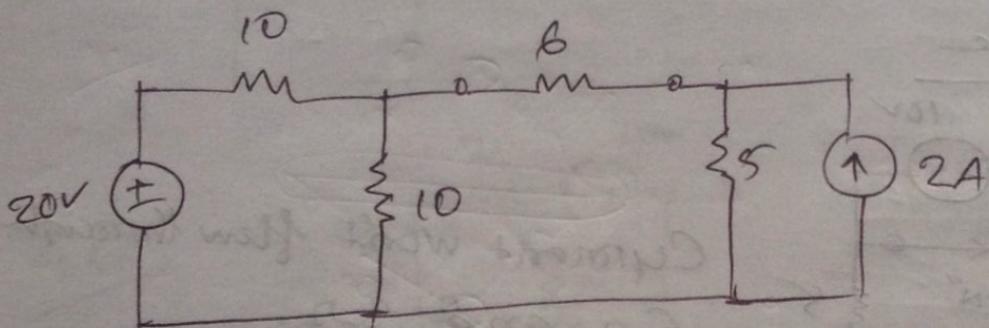


R_{Th}

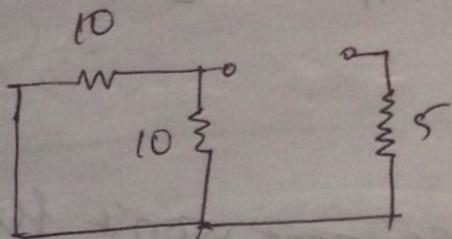

$$R_{Th} = (10 \parallel 10) + 5 \\ = 10\Omega$$

V_{Th}
When 20V is active

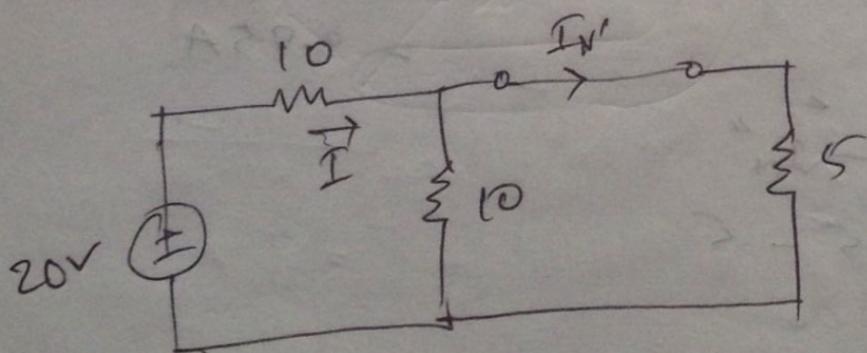


$$R_{eq} = (10 \parallel 5) + 10 \\ = \frac{40}{3}\Omega$$


$$\therefore I = \frac{20}{\frac{40}{3}} = 1.5A$$

$$\therefore \overrightarrow{I_H'} = I_{S2} = \frac{10 \times 1.5}{10+5} = 1A$$

When 2A is active

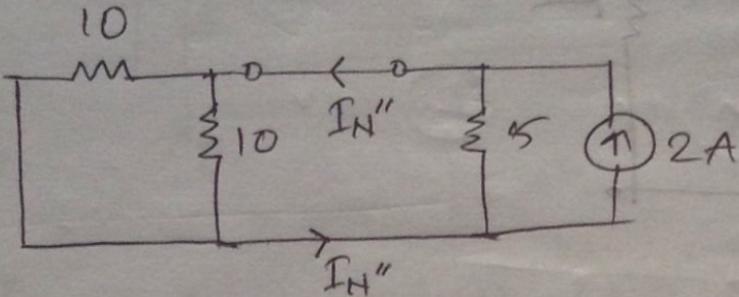


$$10 \parallel 10 = 5\Omega$$

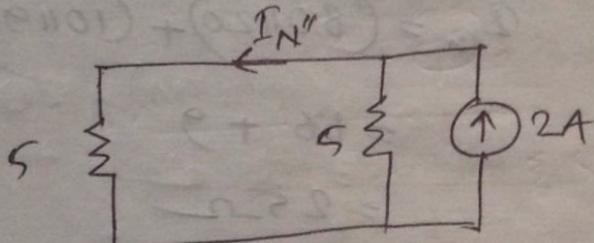

$$I_H'' = \frac{5 \times 2}{5+5} = 1A$$

$$\therefore I_H = I_H' - I_H'' = 1 - 1 = 0A$$


$$\therefore V_{TH} = I_H R_{TH} = 0V$$

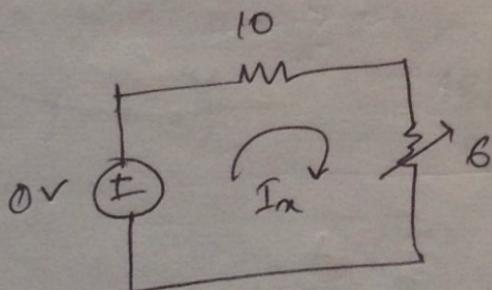


$$I_H = \frac{0}{10+6} = 0A$$

AUT - 15

(3) b)

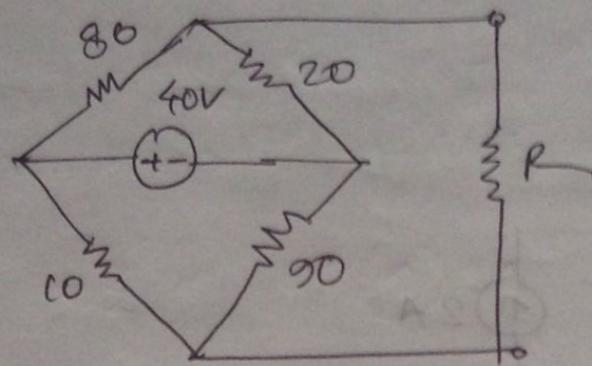


R_{TH}

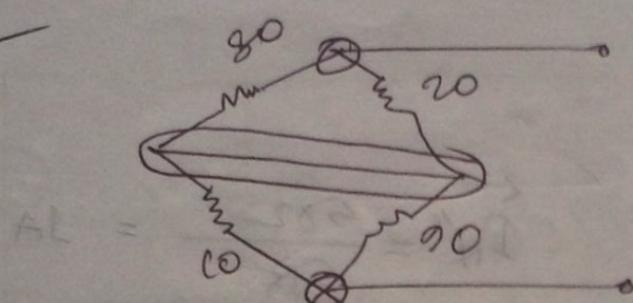


$$\begin{aligned}
 R_{TH} &= (80 \parallel 20) + (10 \parallel 90) \\
 &= 16 + 9 \\
 &= 25 \Omega
 \end{aligned}$$

R must be 25Ω for maximum power.

(Q) V_{TH}

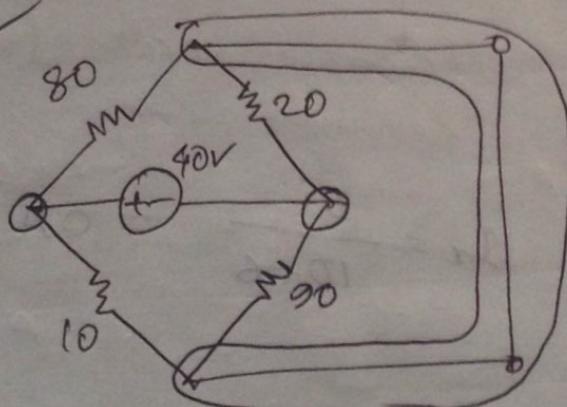

(F) 6

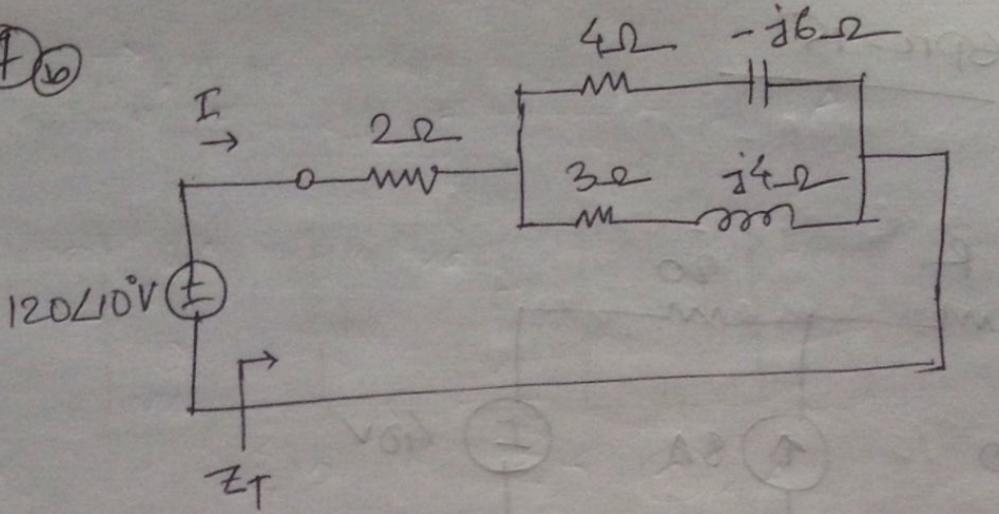

$$Z_T = 2 + \left\{ (4 - j6) \parallel (3 + j4) \right\}$$

$$= 2 + \frac{(4 - j6)(3 + j4)}{4 - j6 + 3 + j4}$$

$$= 2 + \frac{12 - 36 - 2j}{7 - j2}$$

$$= 2 + 4.83 + j1.09$$


$$\therefore Z_T = 6.83 + j1.09$$

$$= 6.92 \angle 9.1^\circ$$


$$\therefore I = \frac{V}{Z_T} = \frac{120 \angle 10^\circ}{6.92 \angle 9.1^\circ} = 17.35 \angle 0.9^\circ \text{ (Am)}$$

SPR-15

(3) (b)

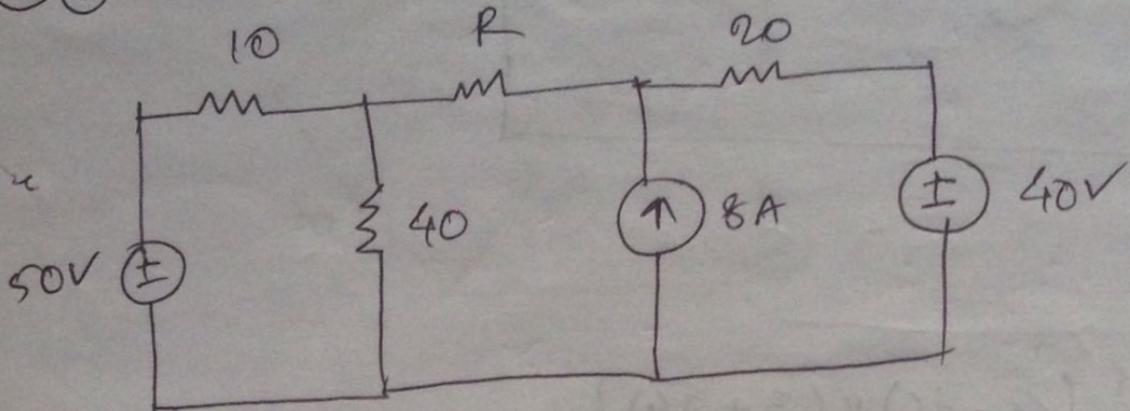


R_{TH}

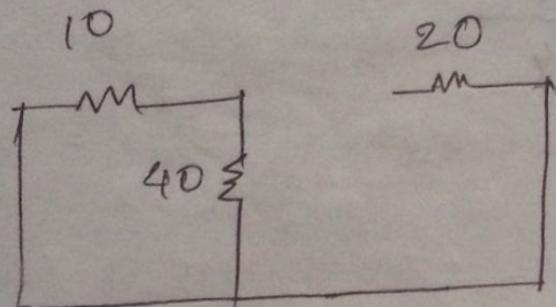

$$R_{TH} = (10 \parallel 40) + 20 \\ = 28 \Omega$$

V_{TH}
When 50V is active

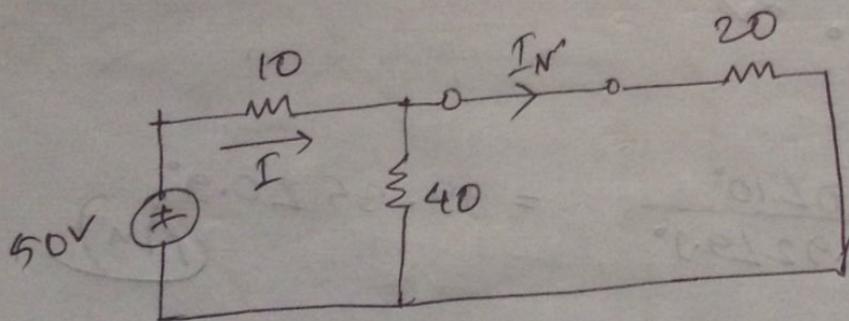


$$R_{eq} = (20 \parallel 40) + 10 \\ = \frac{70}{3} \Omega$$


$$\therefore I = \frac{50}{\frac{70}{3}} = \frac{15}{7} \text{ A}$$

$$\therefore \vec{I}' = I_{20\Omega} = \frac{40 \times \frac{15}{7}}{40 + 20} = \frac{10}{7} \text{ A}$$

When 8A is active

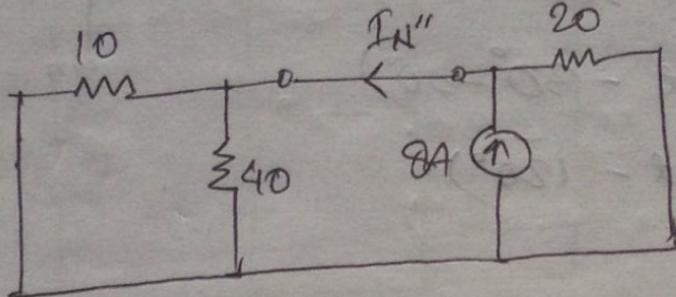


$$10 \parallel 40 = 8\Omega$$

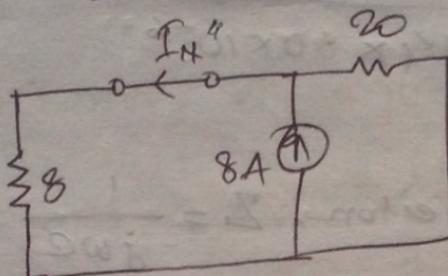

$$\therefore I_N'' = \frac{20 \times 8}{20 + 8} = \frac{40}{7} A$$

When 40V is active

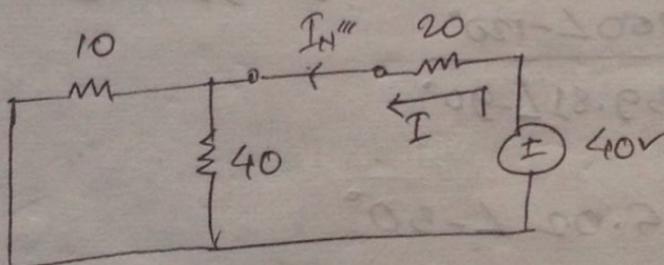

$$R_{eq} = (10 \parallel 40) + 20 \\ = 28\Omega$$

$$\therefore I = \frac{40}{28} = \frac{10}{7} A$$

$$\therefore I_N''' = I = \frac{10}{7} A$$

$$\therefore I_H = I_N''' + I_N'' - I_H' \\ = \frac{10}{7} + \frac{40}{7} - \frac{10}{7}$$

$$\therefore I_N = \frac{40}{7} A$$

$$\therefore V_{th} = I_H \times R_{th} \\ = \frac{40}{7} \times 28 \\ = 160 V$$

$$P_{max} = \frac{V_{th}^2}{4R_{th}} = 228.57 V$$

An.


Nayeem Mahmood / 1AM / C161026

Q7@

$$V = 200 \sin(314t - 30^\circ)$$

$$= 200 \cos(314t - 30^\circ - 90^\circ)$$

$$= 200 \cos(314t - 120^\circ)$$

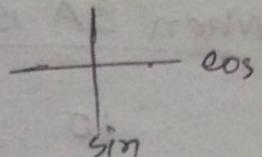

$$\omega = 314 \text{ rad/s}$$

$$\text{Reactance} = \frac{1}{\omega C} = \frac{1}{314 \times 80 \times 10^{-6}} = 39.81 \Omega$$

$$\text{Impedance of } 80\text{fF capacitor}, Z = \frac{1}{j\omega C}$$

$$= -j39.81 \Omega$$

$$= 39.81 \angle -90^\circ$$


$$\therefore I = \frac{V}{Z} = \frac{200 \angle -120^\circ}{39.81 \angle -90^\circ}$$

$$= 5.02 \angle -30^\circ$$

$$= 5.02 \cos(314t - 30^\circ)$$

(Ans)

(5)

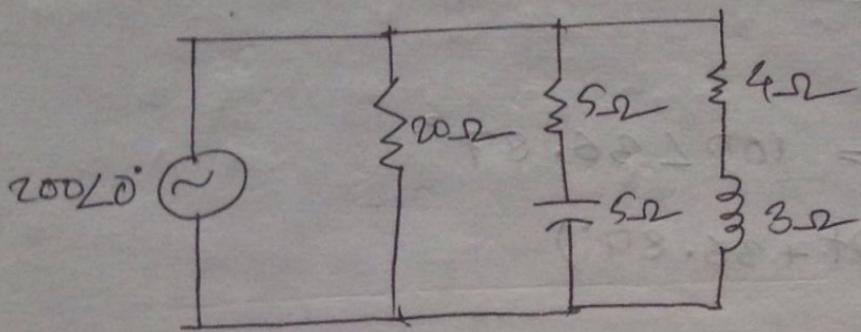

Ques 47

$$\begin{aligned}
 \text{Total Impedance, } Z_T &= \{(4+3) \parallel (5+5)\} \parallel 2\Omega \\
 &= (7 \parallel 10) \parallel 2\Omega \\
 &= \frac{140}{41} \Omega = \frac{140}{41} \angle 0^\circ
 \end{aligned}$$

$$\text{Total Admittance, } Y = \frac{1}{Z_T} = \frac{41}{140} \text{ S}$$

$$\therefore \text{Total current} = \frac{200\angle 0^\circ}{\frac{140}{41}\angle 0^\circ} = 58.57\angle 0^\circ$$

Power supplied by source,

$$\begin{aligned}
 P &= \frac{V^2}{R Z_T} = \frac{(200\angle 0^\circ)^2}{\frac{140}{41}\angle 0^\circ} = 11.71 \text{ kW} \\
 &\quad (\text{Ans})
 \end{aligned}$$

Aut-14

(+) @

$$V = 80 + j60^\circ = 100 \angle 36.87^\circ$$

$$= 100 \cos(\omega t + 36.87^\circ)$$

$$I = -4 + j10^\circ = 2\sqrt{29} \angle 111.80^\circ$$

$$= 2\sqrt{29} \cos(\omega t + 111.80^\circ)$$

Impedance, $Z_T = \frac{V}{I} = 9.28 \angle -74.93^\circ$

$$P = \frac{V^2}{Z_T} = 1077 \angle 148.67 \text{ W}$$

$$Q = V I \sin \phi = \frac{100 \times 100}{\sqrt{2}} \times \sin(111.80^\circ) = 10000 \text{ Var}$$

$$W = V I P \cos \phi = \frac{100 \times 100}{\sqrt{2}} \times \cos(111.80^\circ) = 10000 \text{ J}$$