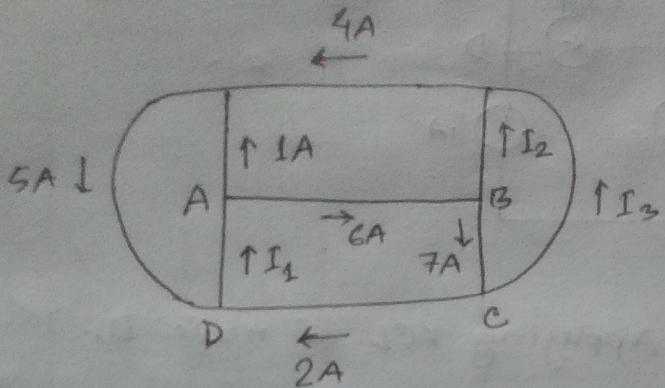


EEE-1105

(2.9)




Applying KCL at node D, || Applying KCL at node B,

$$I_1 = 5+2 = 7A \quad || \quad I_2 + 7 = 6 ; \therefore I_2 = -1A$$

Applying KCL at node C,

$$I_3 + 2 = 7 ; \therefore I_3 = 5A$$

(2.10)

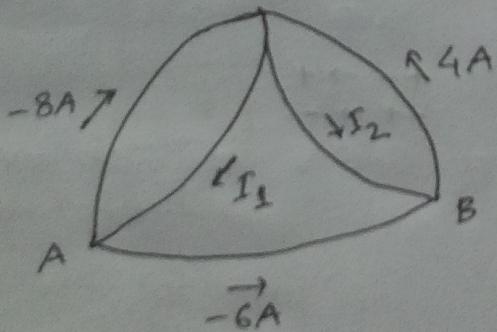


Applying KCL at node A,

$$I_1 = -8 - 6 = -14A$$

Applying KCL at node B,

$$I_2 - 6 = 4 = 6 + 4 = 10A$$

2.13

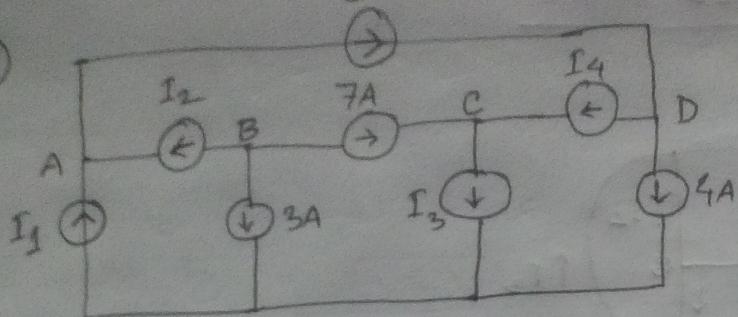

Applying KCL at node B,

$$I_2 + 3 + 7 = 0$$

$$\therefore I_2 = -10 \text{ A}$$

Applying KCL at node A,

$$I_1 + I_2 = 2$$

$$\Rightarrow I_1 = 2 - I_2 = 2 + 10$$

$$\therefore I_1 = 12 \text{ A}$$

Applying KCL at node D,



$$I_4 + 4 = 2 \quad ; \quad \therefore I_4 = -2 \text{ A}$$

Applying KCL at node C,

$$I_3 = I_4 + 7 = -2 + 7$$

$$\therefore I_3 = 5 \text{ A}$$

2.14

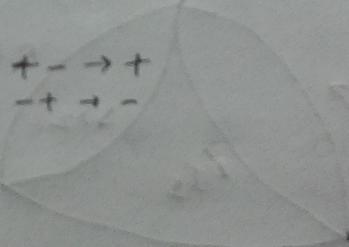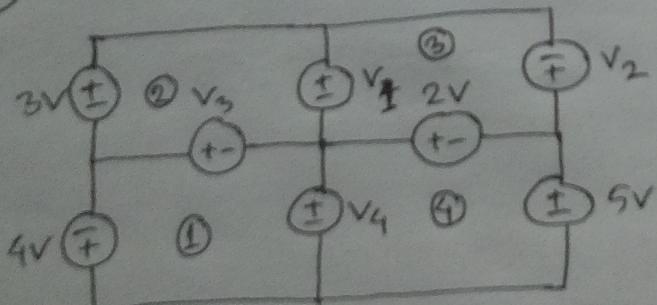

Applying KVL at loop 4,

$$-V_4 + 2 + 5 = 0$$

$$\therefore V_4 = 7 \text{ V}$$

Applying KVL at loop 1,

$$4 + V_3 + V_4 = 0$$

$$\therefore V_3 = -4 - V_4 = -4 - 7$$

$$\therefore V_3 = -11 \text{ V}$$


Applying KVL at loop 2,

$$-3 + V_1 - V_3 = 0 \quad \Rightarrow V_1 = V_3 + 3$$

$$\therefore V_1 = -8 \text{ V}$$



Applying KVL at loop 3,
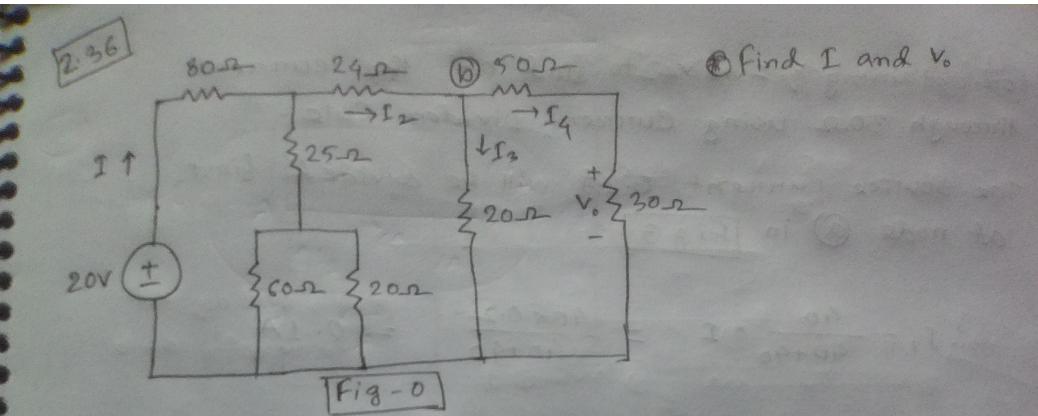
$$-V_2 - V_3 - 2 = 0 \quad \Rightarrow V_2 = -V_3 - 2$$



For obtaining I , we've to find out R_{eq} first

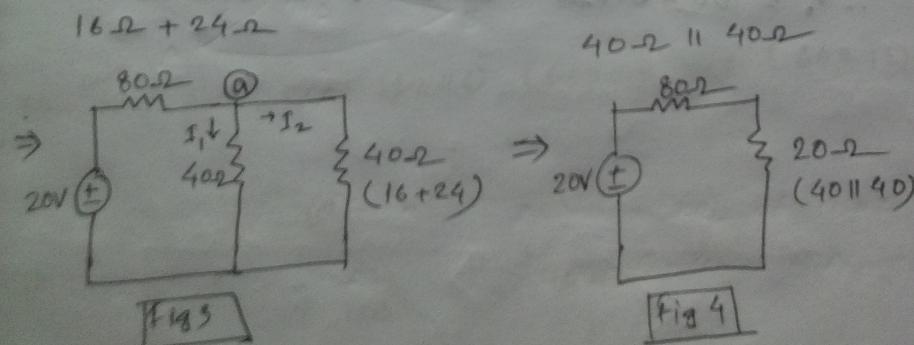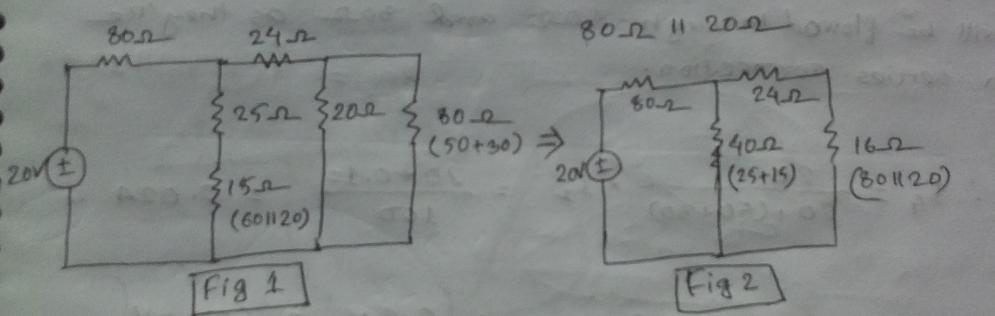$\therefore 30\Omega$ and 50Ω are in series.



$$\therefore R_{eq} = 80 + 20 = 100\Omega$$

$$\therefore I = \frac{20}{100} = 0.2A$$

For obtaining V_o , we've to find out the current through 30Ω using Current Divider Rule.


The source current $0.2A$ will be divided first at node \textcircled{a} in Fig 3

$$\therefore I_2 = \frac{40}{40+40} \times I = \frac{40 \times 0.2}{40+40} = 0.1A$$


Current I_2 will be divided into I_3 and I_4 at node \textcircled{b} shown in Fig 0. The same current I_4 will be flowed through 50Ω and 30Ω as they're in series connection.

$$\therefore I_4 = \frac{20}{20+(50+30)} \times I_2 = \frac{20 \times 0.1}{100} = 0.02A$$

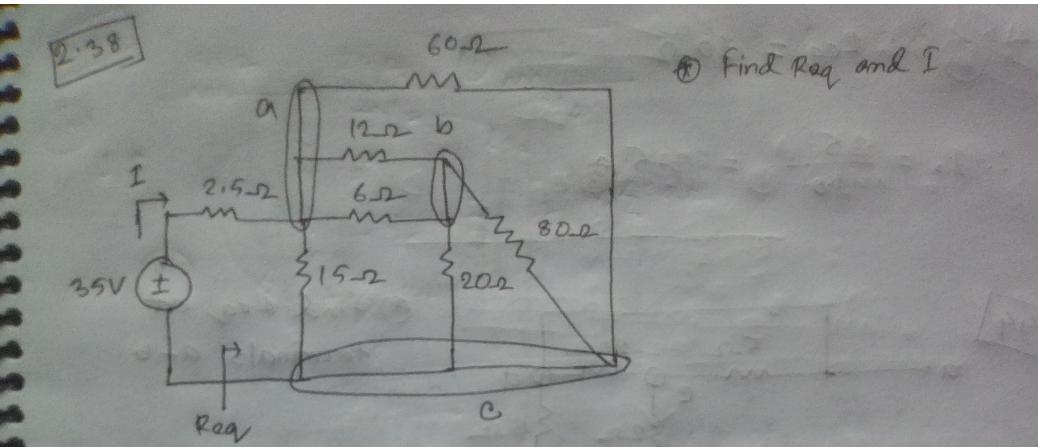
$$\therefore V_o = 30 \times 0.02 = 0.6V = 600mV$$



The circuit is simplified and redrawn

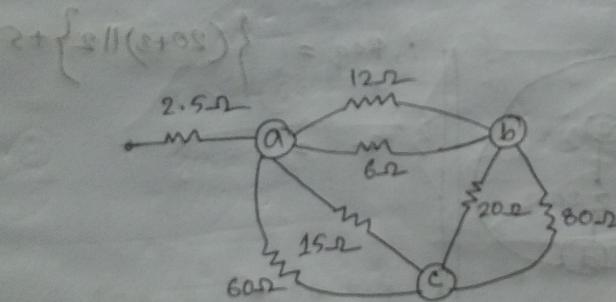

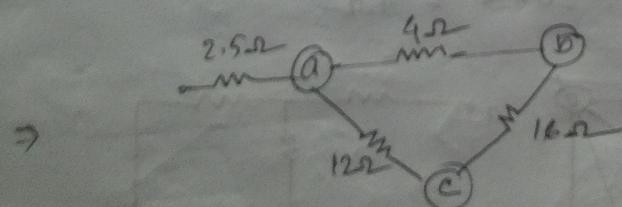Now, it is clear that $(12 \parallel 6)$, $(80 \parallel 20)$ and $(60 \parallel 15)$



Nayeem Mahmood / 1AM / C161026



4 and 16 are in series with parallel to 12

$$\therefore R_{eq} = \left\{ (4+16) \parallel 12 \right\} + 2.5$$

$$\therefore R_{eq} = 10 \Omega$$



$$I_0 = \frac{35}{10} = 3.5 \text{ A}$$

2.45 (a)

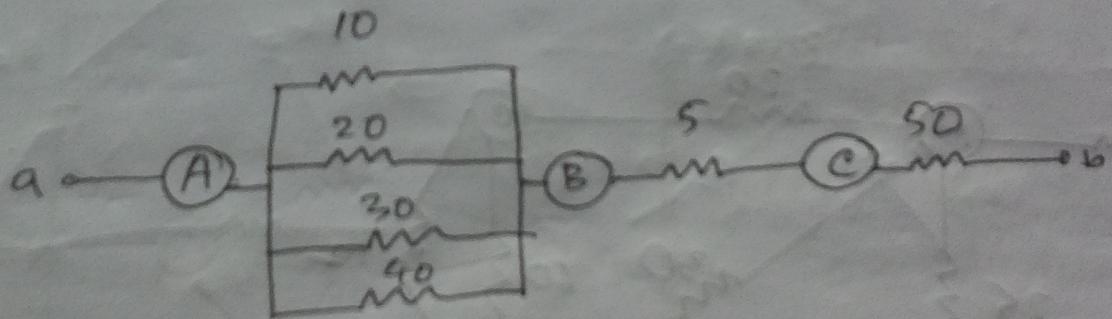
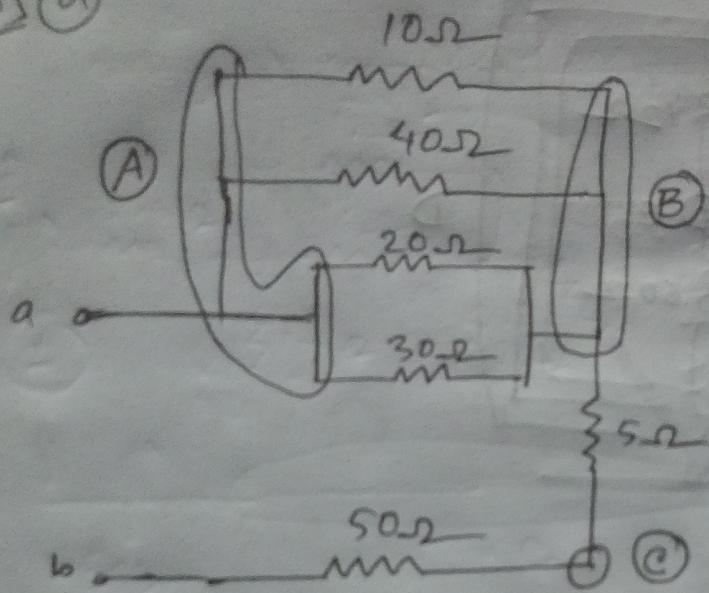


$$\begin{aligned} R_{eq} &= 5 + 50 + \{ 10 \parallel 20 \parallel 30 \parallel 40 \} \\ &= 59.8 \Omega \end{aligned}$$

2.45
b

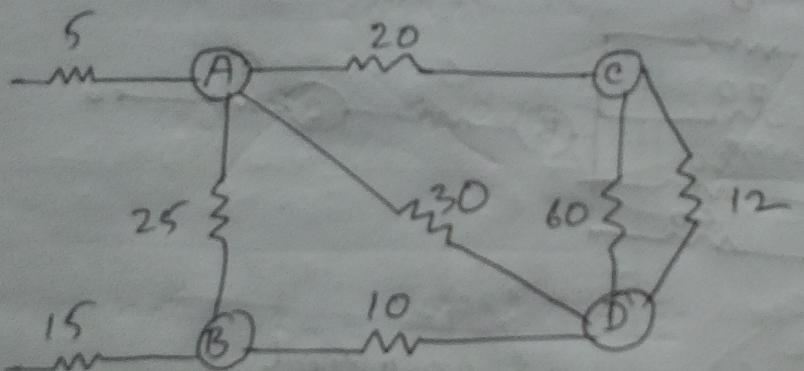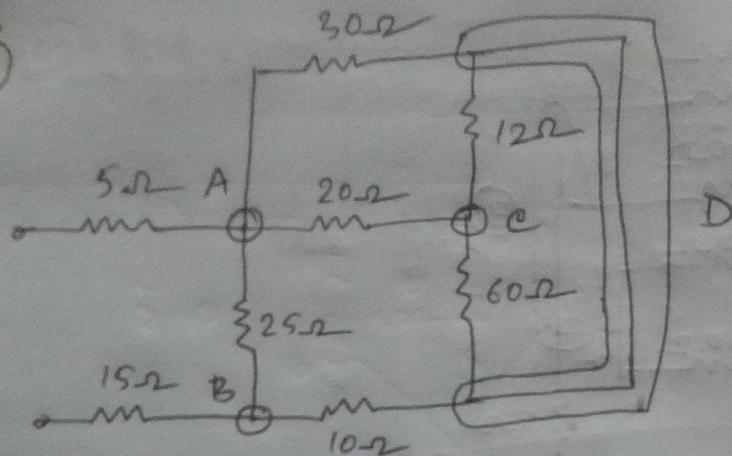


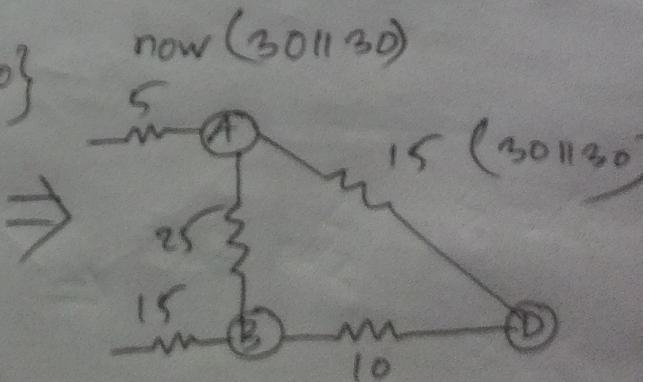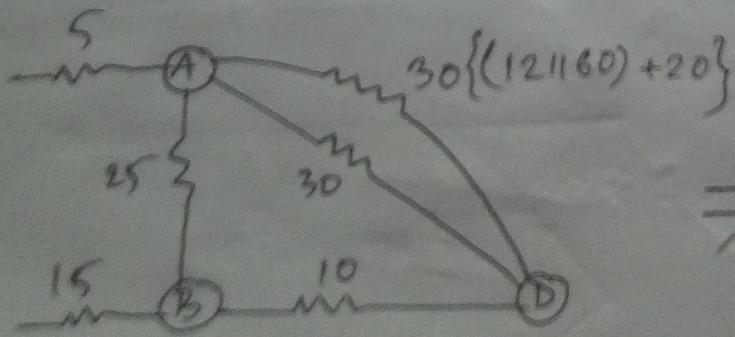12 and 60 in parallel those with one in series with 20.



Now, (15 and 10 in series) \rightarrow Parallel with 25


Nayeem Mahmood / 1AM / C161026

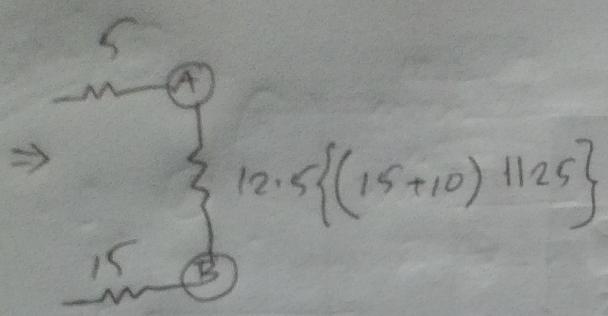

$$\therefore R_{eq} = 5 + 12.5 + 15$$

$$= 32.5 \Omega$$

2.47

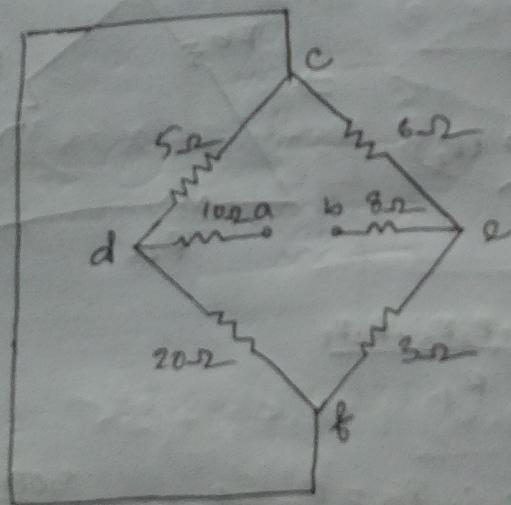

5 and 20 are in parallel that is series with 10

$$\therefore R_{eq'} = (5 || 20) + 10$$

$$= 14 \Omega$$

6 and 3 are in parallel that is series with 8


$$\therefore R_{eq''} = (6 || 3) + 8$$

$$= 10 \Omega$$


$R_{eq'}$ and $R_{eq''}$ are in series.

$$R_{eq} = 14 + 10$$


$$= 24 \Omega$$

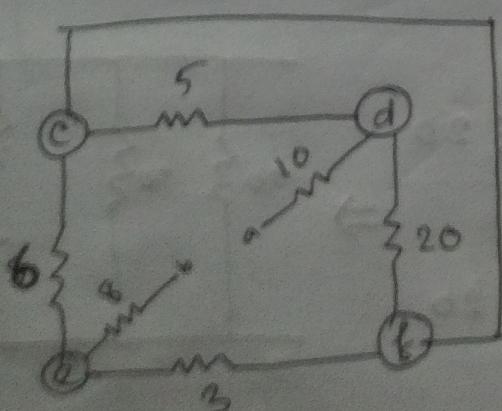

2.51

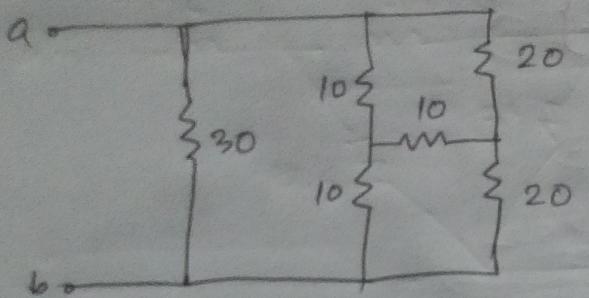


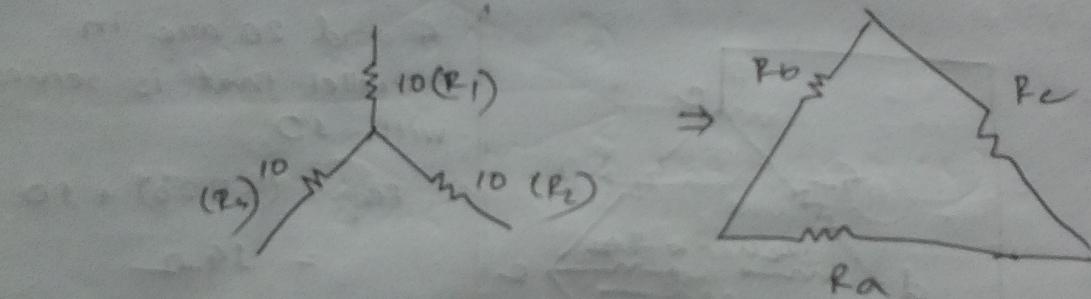
Applying $\Delta \rightarrow Y$ approach in this section



$$\text{We know that, } R_a = \frac{R_1(R_2 + R_3)}{R_1 + R_2 + R_3}$$
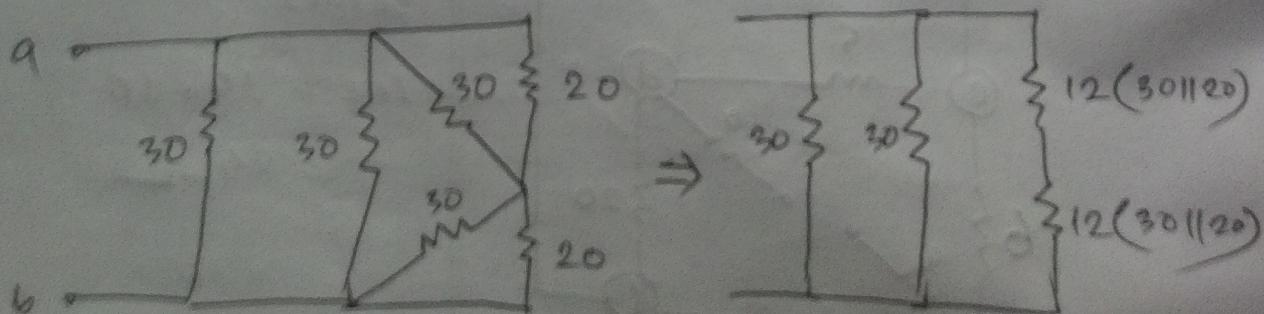
$$\text{Hence, } R_1 = R_2 = R_3 = 10 \Omega ; \therefore R_a = R_b = R_c = \frac{10 \times 10}{10 + 10 + 10} = 3.33 \Omega$$



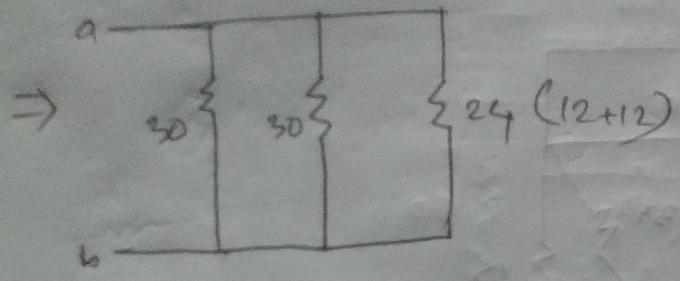


$$\therefore R_{eq} = 30 \parallel 30 \parallel 24$$


$$= \frac{30 \cdot 30 \cdot 24}{(30+30)+24}$$

$$= 9.231 \Omega$$

2.51(b)

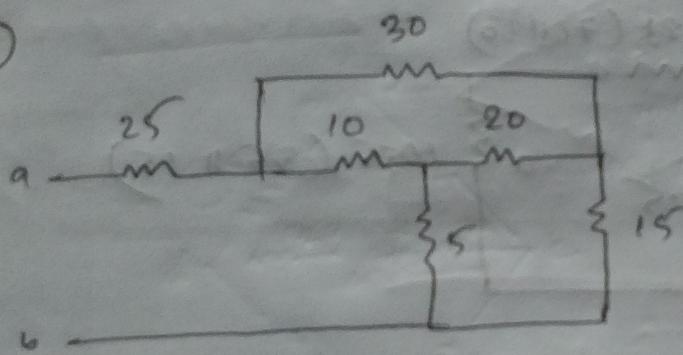

$Y \rightarrow \Delta$ Approach

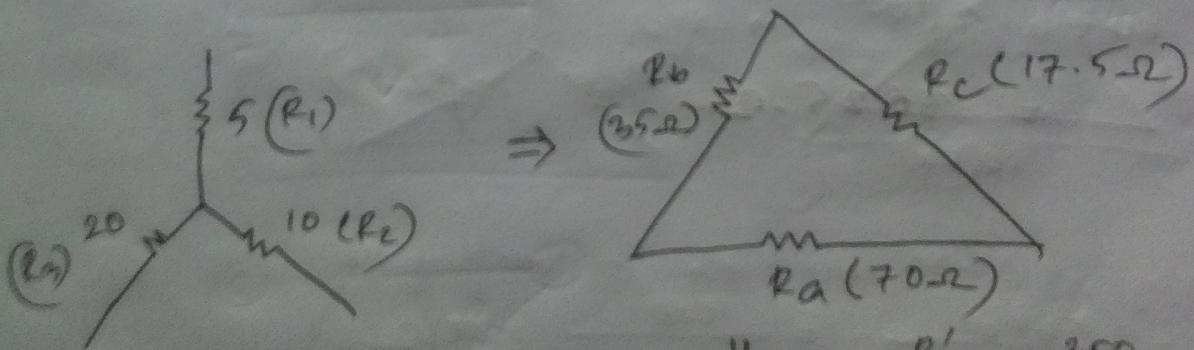


$$\text{Hence, } R' = R_1R_2 + R_2R_3 + R_3R_1$$

$$= 350$$


$$\therefore R_a = \frac{R'}{R_1} = \frac{350}{5} = 70 \Omega$$

$$R_b = \frac{R'}{R_2} = \frac{350}{10} = 35 \Omega$$
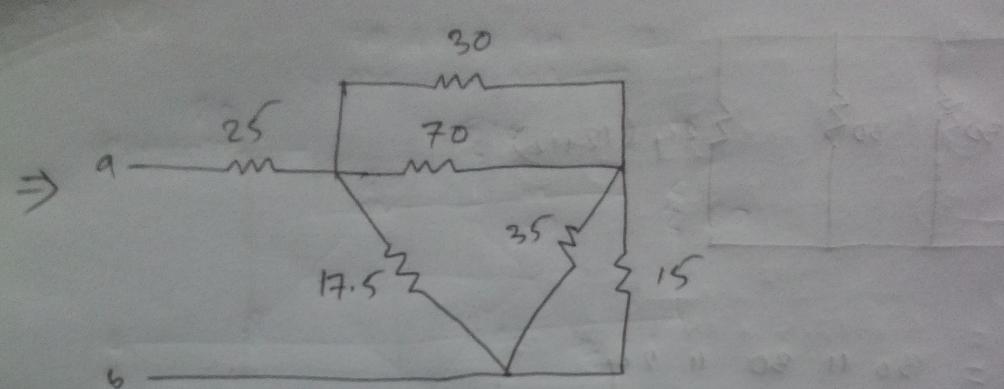
$$R_c = \frac{R'}{R_3} = \frac{350}{20} = 17.5 \Omega$$



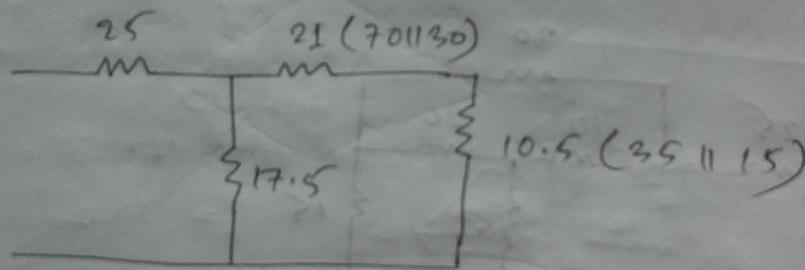
$(70 \parallel 30)$ and $(35 \parallel 15)$




$$\therefore R_{eq} = \left\{ (21 + 10.5) \parallel 17.5 \right\} + 25$$

$$\approx 36.25 \Omega$$


2.43 (a)

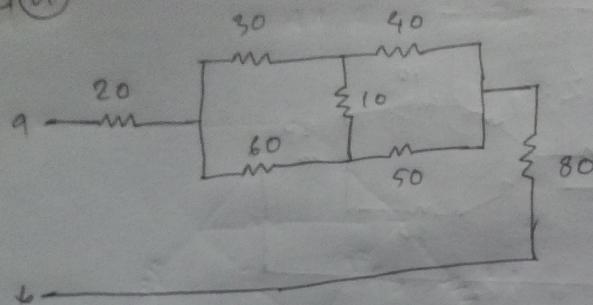

this circuit looks like this

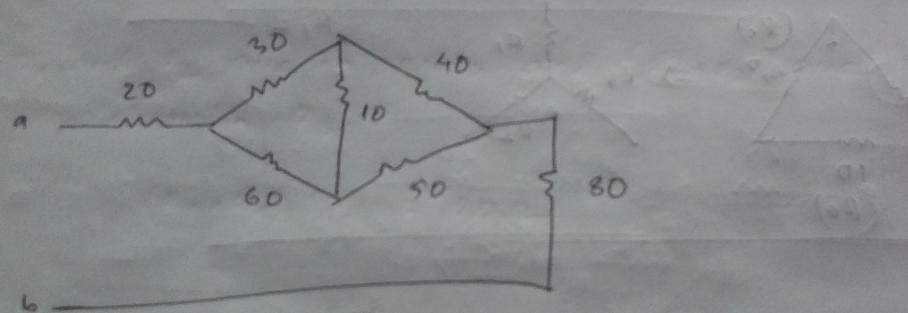

Applying Δ - γ approach,

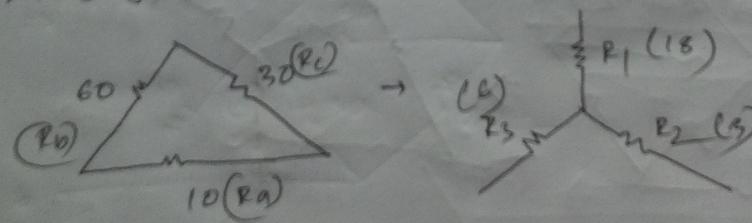


$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c} = \frac{1800}{100} = 18\Omega$$

Nayeem Mahmood / 1AM / C161026

$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c} = \frac{300}{100} = 3\Omega$$
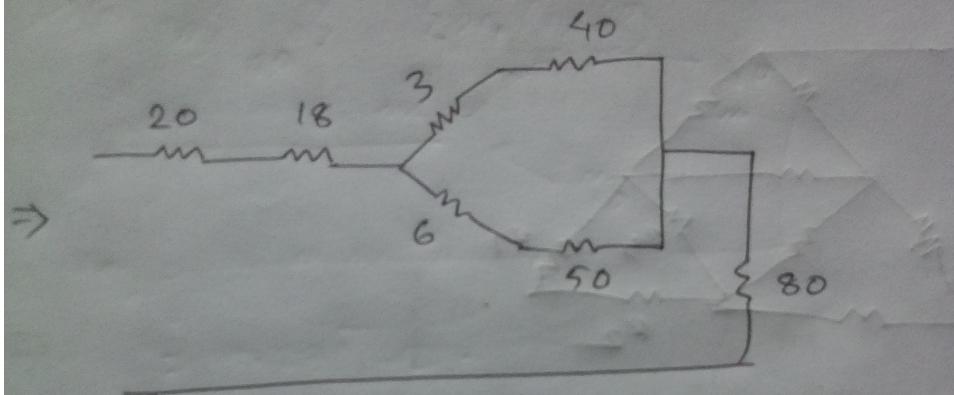
$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c} = \frac{600}{100} = 6 \Omega$$



$$\underline{\underline{R_{eq}'}} = (30 + 40) \parallel (6 + 50)$$

$$= \frac{2408}{99} \Omega$$


$$\therefore R_{eq} = 20 + 18 + \frac{2408}{99} + 80$$

$$= 142.323 \Omega$$

2.53

b


$$AU R = 30\Omega$$

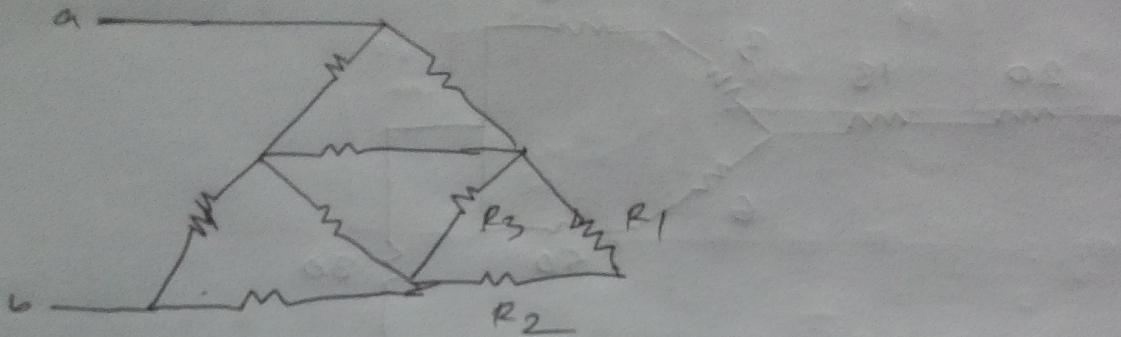


R_1 and R_2 are in series and $(R_1 + R_2)$ are in parallel with R_3 .

$$(R_1 + R_2) \parallel R_3 = 20\Omega$$


b

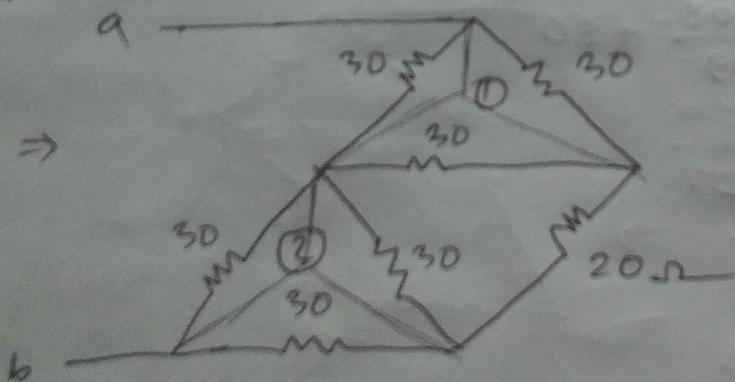

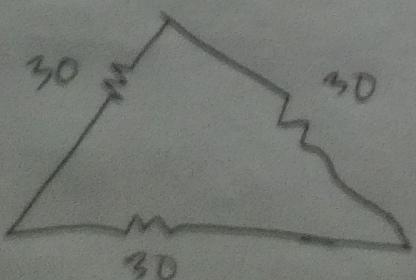Applying $\Delta \rightarrow Y$ approach in section ① and ②




\Rightarrow

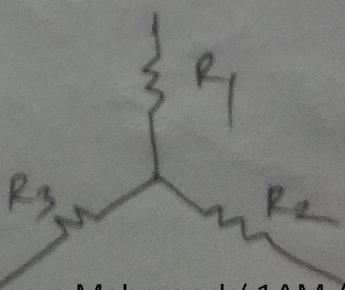


$$\text{Hence } R_a = R_b = R_c = 30\Omega$$

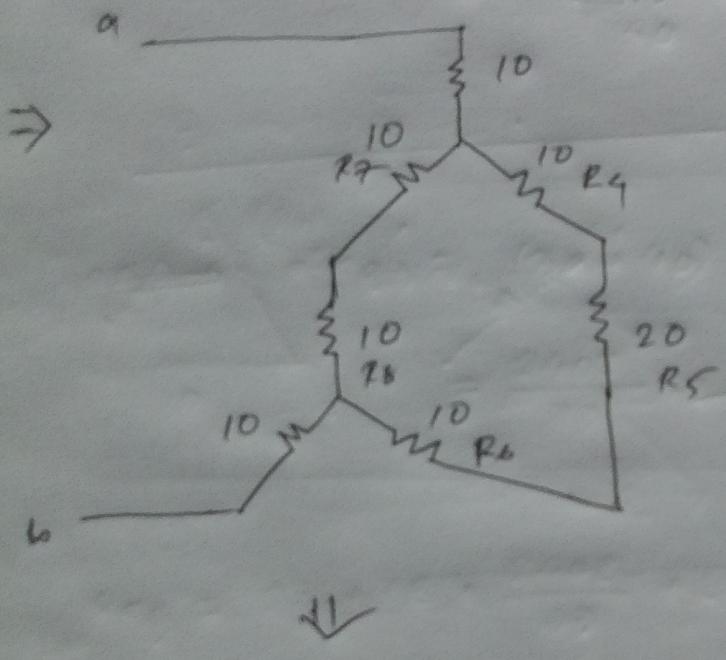
$$\therefore R_1 = R_2 = R_3 = \frac{30 \times 30}{30 + 30 + 30} = 10\Omega$$




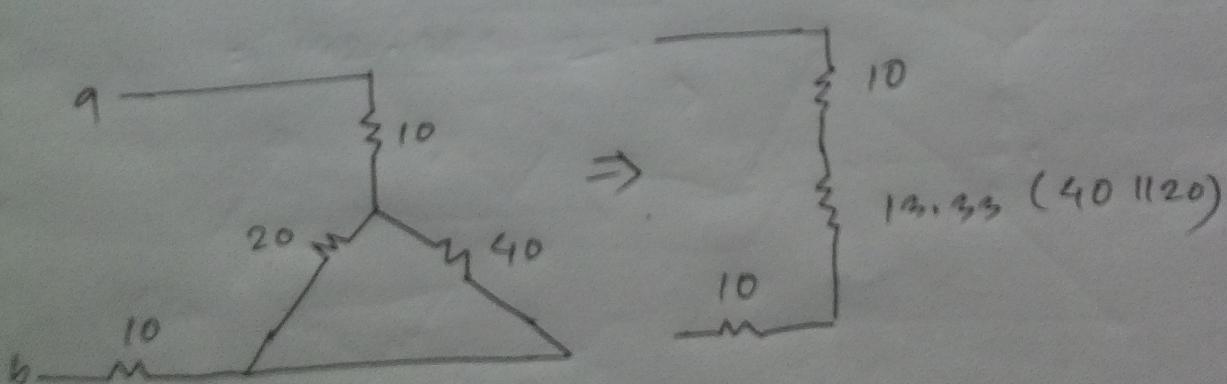R_4, R_5, R_6 in series
 R_7, R_8 in series
 They are in parallel


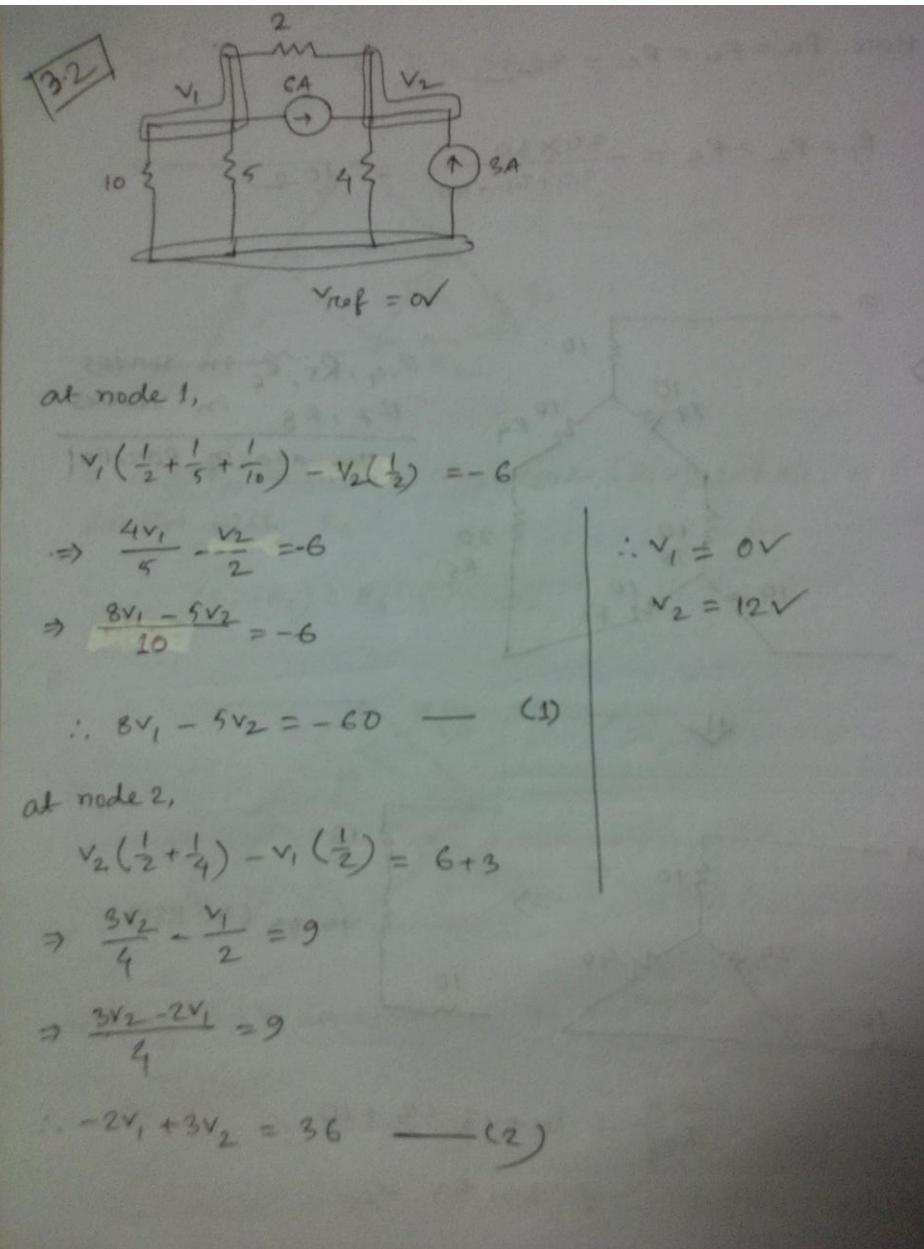
$$\therefore R_{eq} = 10 + 13.33 + 10 \\ = 33.33 \Omega$$



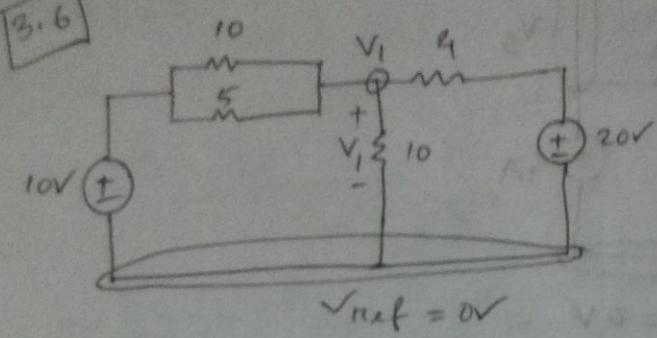

* Without Source Transformation

There are four resistors - 4, 5, 10, 10. All are connected to node V_1 . But on the left side, 10 and 5 are connected to 10V and on the right side 4 is connected to 20V.


Using node analysis,

$$V_1 \left(\frac{1}{4} + \frac{1}{5} + \frac{1}{10} + \frac{1}{10} \right) - 10 \left(\frac{1}{5} + \frac{1}{10} \right) - 20 \left(\frac{1}{4} \right) = 0$$

$$\Rightarrow \frac{13V_1}{20} - 3 - 5 = 0$$


$$\therefore V_1 = 12.308 V$$

* Using Source Transformation

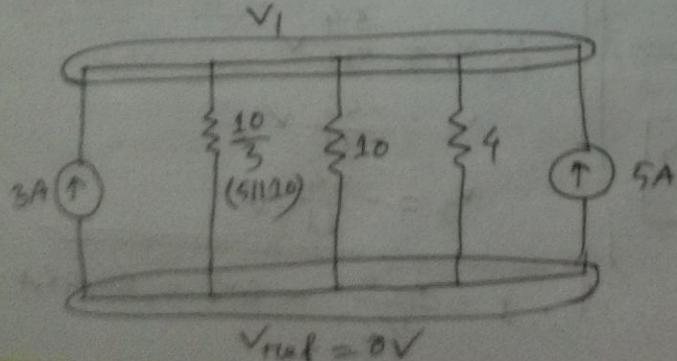


$$\Rightarrow V_1 \left(\frac{1}{4} + \frac{1}{10} + \frac{3}{10} \right) = 5 + 3$$

$$\therefore V_1 = 12.308 V$$

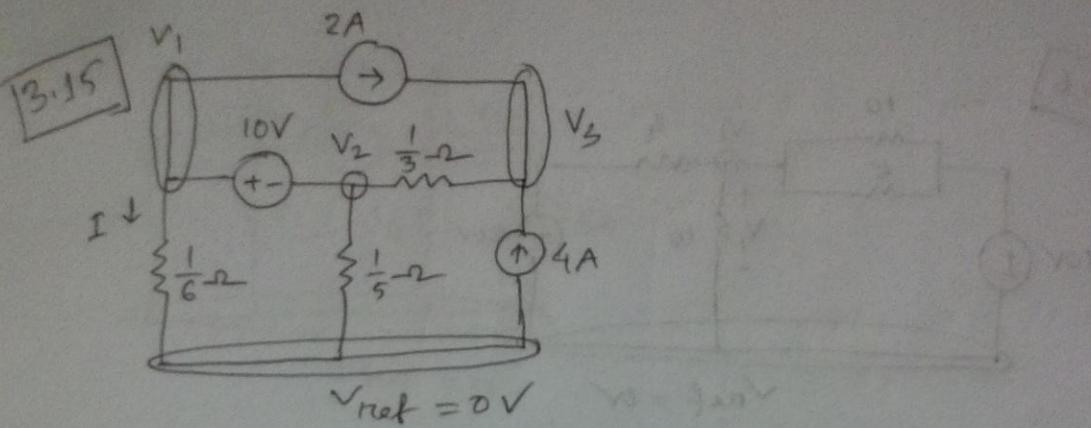

V_1 and V_2 form a supernode.

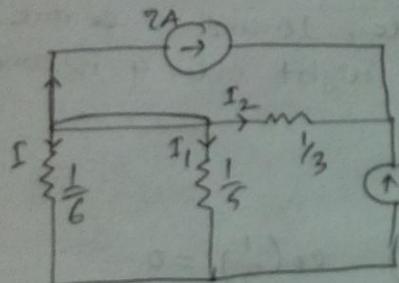

Applying KCL at supernode,

$$\Rightarrow I + I_1 + I_2 + 2 = 0$$

$$\Rightarrow \frac{V_1 - 0}{1/6} + \frac{V_2 - 0}{1/5} + \frac{V_2 - V_3}{1/3} + 2 = 0$$

$$\Rightarrow 6V_1 + 5V_2 + 3V_2 - 3V_3 = -2$$

$$6V_1 + 8V_2 - 3V_3 = -2 \dots (1)$$

Applying KCL at node 3,

$$I_2 + 4 + 2 = 0$$

$$\Rightarrow \frac{V_2 - V_3}{1/3} = -6$$

$$\Rightarrow 3V_2 - 3V_3 = -6 \dots (2)$$

From supernode,


$$V_1 - V_2 = 10 \dots (3)$$


$$\therefore V_1 = \frac{54}{11} V$$

$$V_2 = \frac{-56}{11} V$$


$$V_3 = -\frac{34}{11} V$$

$$\therefore I = \frac{V_1 - 0}{1/6} = 6V_1 = 29.45 A$$

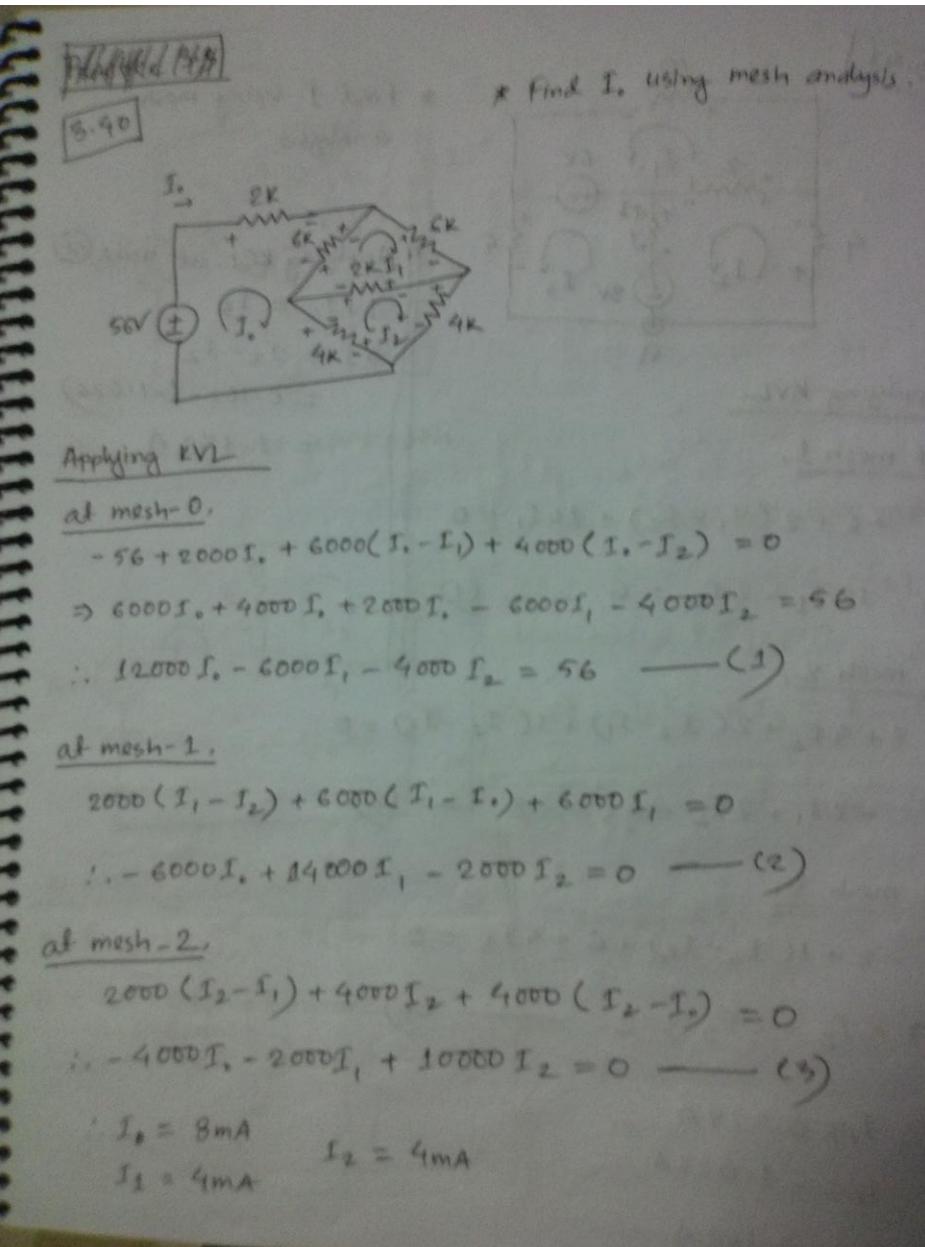

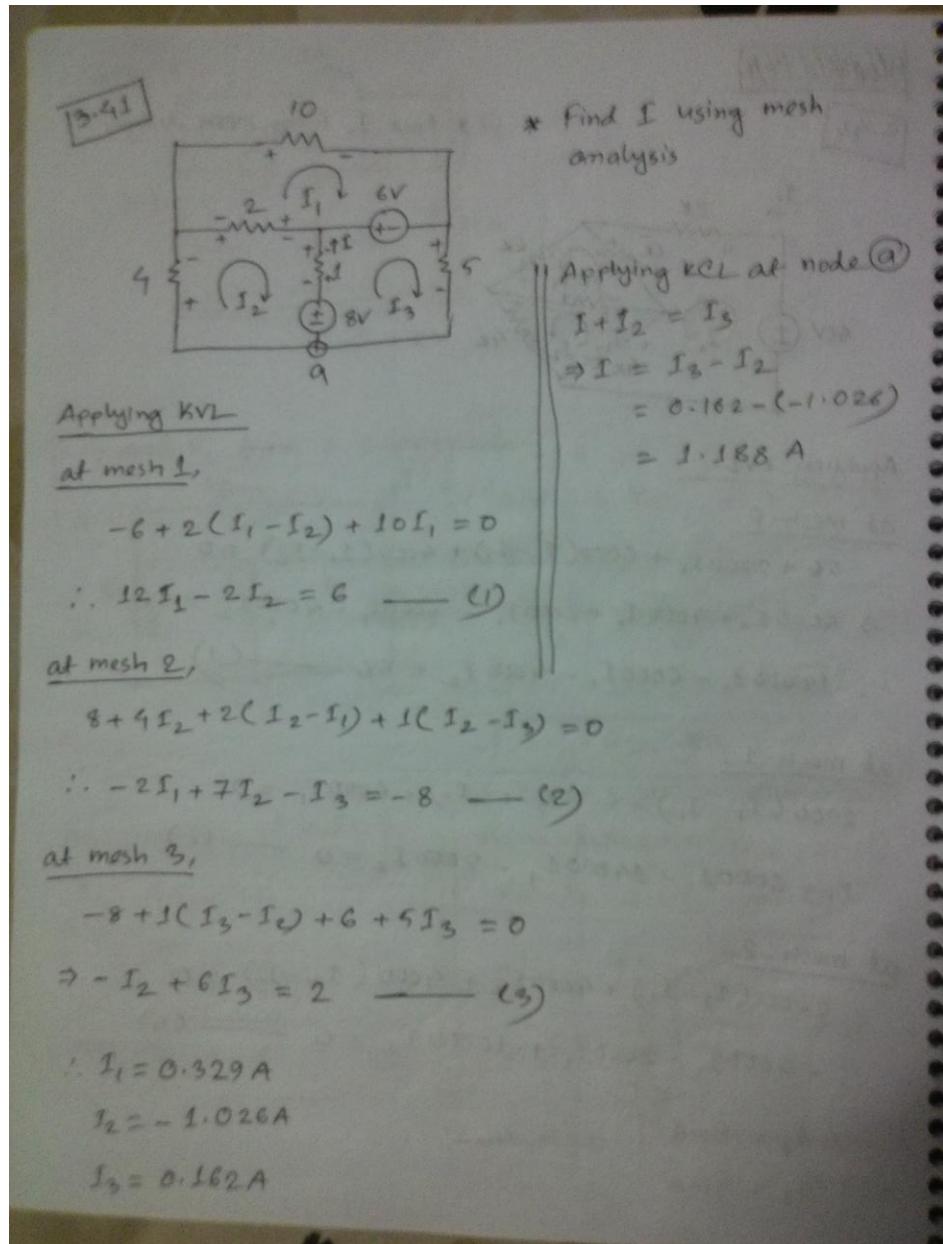

Practice 3.7

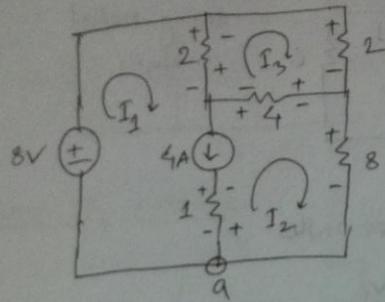

Using supermesh approach,

\Rightarrow Applying KVL at supermesh.

$$\begin{aligned} -8 + 2(I_1 - I_3) + 4(I_2 - I_3) \\ + 8I_2 = 0 \\ \Rightarrow 2I_1 + 12I_2 - 6I_3 = 8 \quad (1) \end{aligned}$$

Applying KCL at node \textcircled{a}

At mesh 3


$$2(I_3 - I_1) + 2I_3 + 4(I_3 - I_2) = 0$$

$$\Rightarrow -2I_1 - 4I_2 + 8I_3 = 0$$

$$\therefore I_1 + 2I_2 - 4I_3 = 0 \quad (2)$$


$$\begin{aligned} I_2 + 4 = I_1 \\ \therefore I_1 - I_2 = 4 \quad (3) \\ \therefore I_1 = 4.632 \text{ A} \\ I_2 = 0.632 \text{ A} \\ I_3 = 1.474 \text{ A} \end{aligned}$$

Practice 3.3

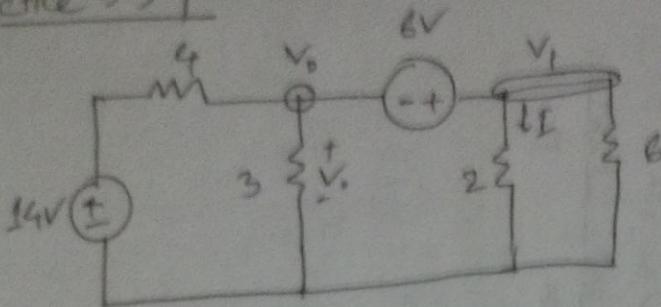

* find V_0 and I using nodal analysis

V_0 and V_1 nodes form a supernode

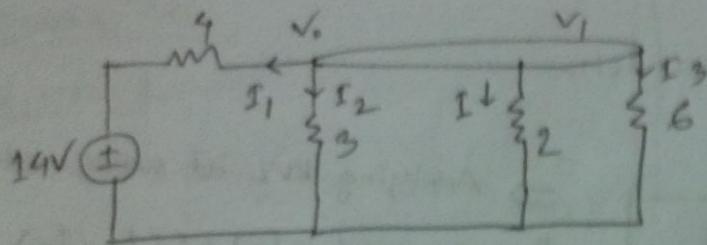

Applying KCL at supernode,

$$I_1 + I_2 + I_3 + I = 0$$

$$\Rightarrow \frac{V_0 - 14 - 0}{4} + \frac{V_0}{3} + \frac{V_1}{2} + \frac{V_1}{6} = 0$$

$$\Rightarrow \frac{3V_0 - 42 + 4V_0 + 6V_1 + 2V_1}{12} = 0$$

$$\therefore 7V_0 + 8V_1 = 42 \quad \text{--- (1)}$$

$$\text{and } V_1 - V_0 = 6$$

$$\text{or, } -V_0 + V_1 = 6 \quad \text{--- (2)}$$


$$\therefore V_0 = -0.4V$$

$$V_1 = 5.6V$$

$$\text{and } I = \frac{V_1}{2}$$


$$= \frac{5.6}{2}$$

$$= 2.8A.$$

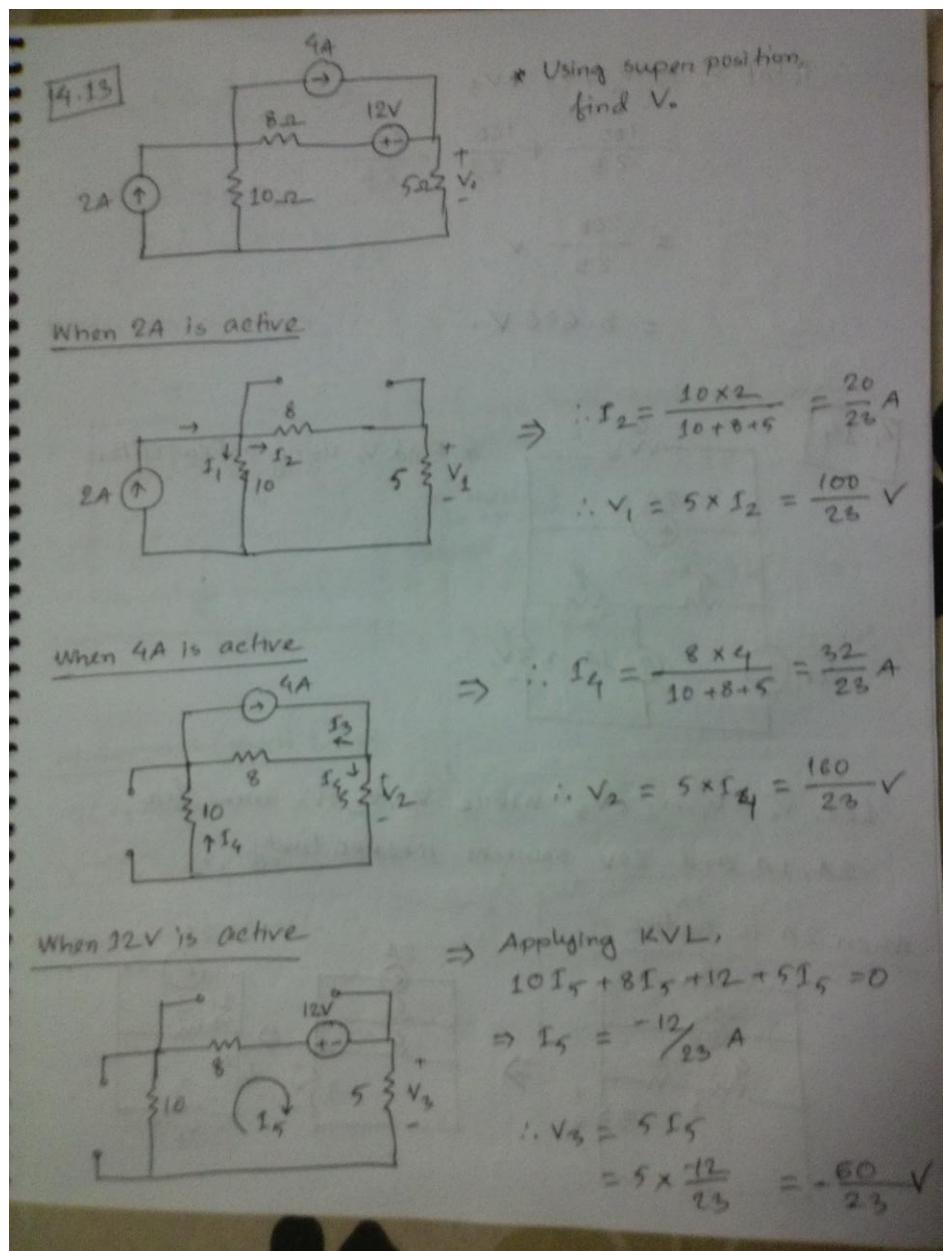

$$\begin{aligned}
 \text{Total } V_o &= V_1 + V_2 + V_3 \\
 &= \frac{100}{23} + \frac{160}{23} - \frac{60}{23} \\
 &= \frac{200}{23} \text{ V} \\
 &= 8.696 \text{ V.}
 \end{aligned}$$


4.14

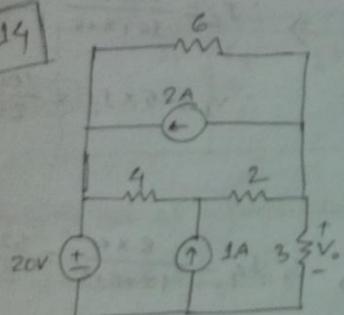

* Find V_o using superposition

Let, $V_o = V_1 + V_2 + V_3$, whence V_1, V_2, V_3 are due
to $2A, 1A$ and $20V$ sources respectively.


When $2A$ is active

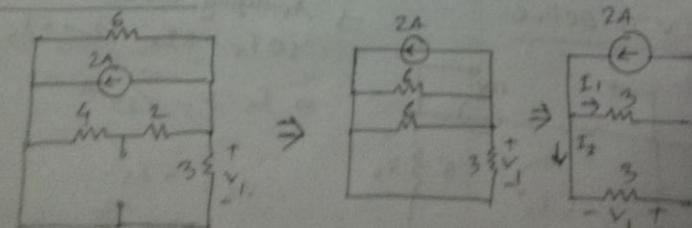

$$\therefore I_2 = -\frac{3 \times 2}{3+3} = -1A$$

$$\therefore V_1 = 3 \times I_2 \\ = -3V$$

When 1A is active

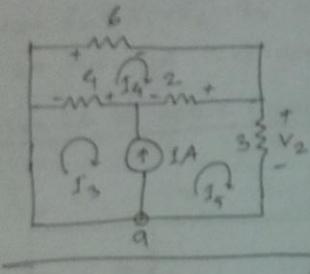

We'll use mesh/supermesh analysis to obtain V_2

At mesh 4

$$\text{Equation} \\ 2(I_4 - I_3) + 4(I_4 - I_5) + 6I_4 = 0 \\ \therefore -4I_3 + 12I_4 - 2I_5 = 0 \quad (1)$$

At supermesh (mesh 3 & 5)

$$4(I_3 - I_4) + 2(I_5 - I_4) + 3I_5 = 0 \\ \Rightarrow 4I_3 - 6I_4 + 5I_5 = 0 \quad (2)$$

applying KCL at node a,

$$I_5 = 1 + I_3$$

$$\therefore I_3 + I_5 = 1 \quad (3)$$

$$\therefore I_3 = -\frac{2}{3}A$$

$$I_4 = -\frac{1}{6}A$$


$$I_5 = \frac{1}{3}A$$

$$\therefore V_2 = 3I_5$$


$$= 3 \times \frac{1}{3}$$

$$= 1V$$

When 20V is active

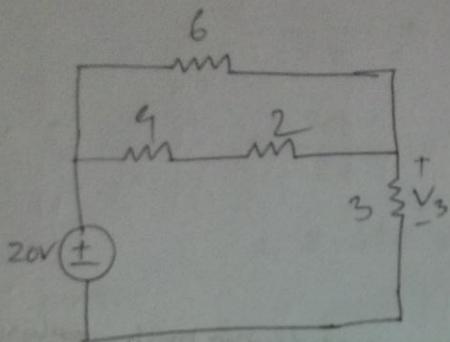


$$(4+2) \parallel 6 = 3\Omega$$

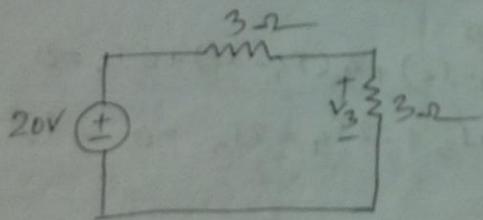

$$\text{Using VDR, } V_3 = \frac{3 \times 20}{3+3} = 10V$$

$$\begin{aligned}\therefore \text{Total } V_o &= V_1 + V_2 + V_3 \\ &= -3 + 1 + 10 \\ &= 8V\end{aligned}$$



Fig. 16

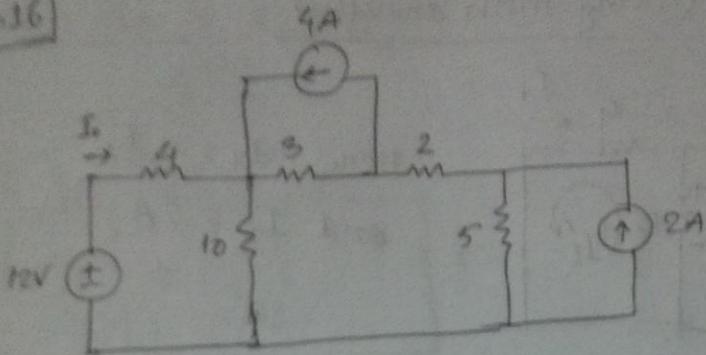

* Find I_3 using superposition analysis.

Let $I_0 = I_1 + I_2 + I_3$ where I_1 , I_2 and I_3 are for 2A, 4A and 12V sources respectively.


When 2A is active (using CDR)

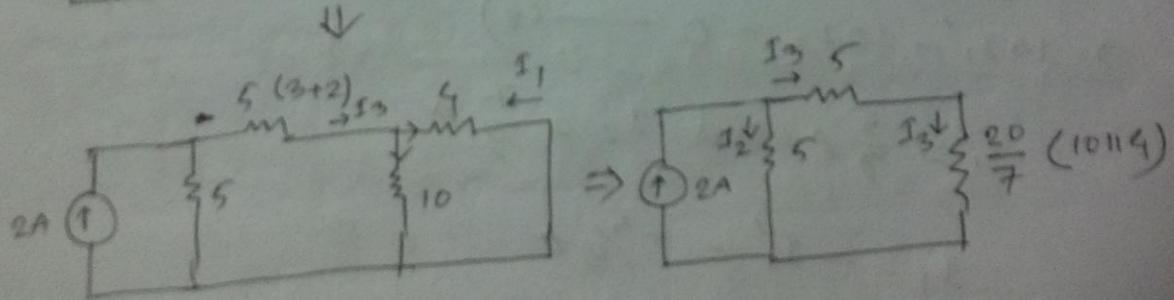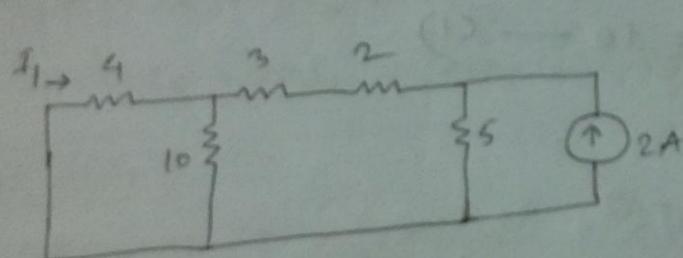

$$\therefore I_3 = \frac{5 \times 2}{5+5+\frac{20}{7}} = \frac{7}{9} A$$

$$\therefore I_1 = \frac{-10 \times \frac{7}{9}}{4+10} = -\frac{7}{9} A$$

When 2A is active (using mesh analysis)

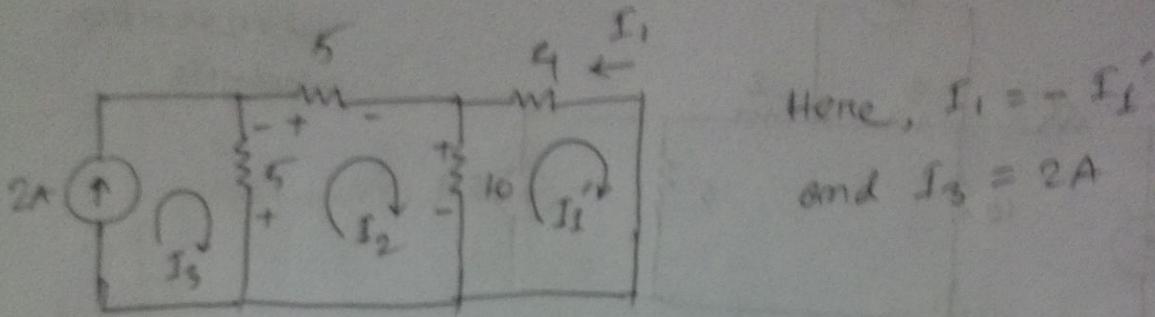

$$\text{Here, } I_1 = -I_1'$$

$$\text{and } I_3 = 2A$$

at mesh 2

$$5(I_2 - I_3) + 5(I_2) + 10(I_2 - I_1') = 0$$

$$\Rightarrow -10I_1' + 20I_2 = 5I_3$$

$$\therefore -10I_1' + 20I_2 = 10 \quad \text{--- (1)}$$

at mesh 1


$$10(I_1' - I_2) + 4I_1' = 0$$

$$\Rightarrow 14I_1' - 10I_2 = 0 \quad \text{--- (2)}$$

$$\therefore I_1' = \frac{5}{9}A \text{ and } I_2 = \frac{7}{9}A$$

$$\therefore I_1 = -I_1' = -\frac{5}{9}A$$

When I_4 is active

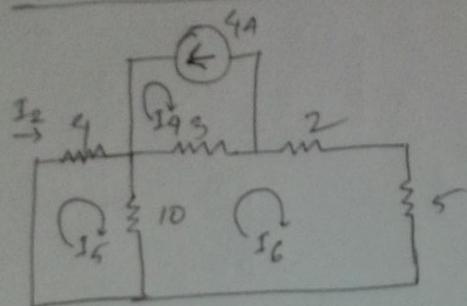

Hence $I_4 = -I_4$
and $I_5 = I_2$

at mesh 6

$$10(I_6 - I_5) + 3(I_6 - I_4) + 2I_6 + 5I_6 = 0$$

$$\Rightarrow -10I_5 + 20I_6 = 3I_4$$

$$\therefore -10I_5 + 20I_6 = -12 \quad \text{--- (1)}$$

at mesh 5


$$4I_5 + 10(I_5 - I_6) = 0$$

$$\Rightarrow 14I_5 - 10I_6 = 0 \quad \text{--- (2)}$$

$$\therefore I_6 = \frac{-2}{3}A \quad \text{and} \quad I_5 = \frac{-14}{15}A$$

$$\therefore I_2 = \frac{-2}{3}A$$

When 12V is active

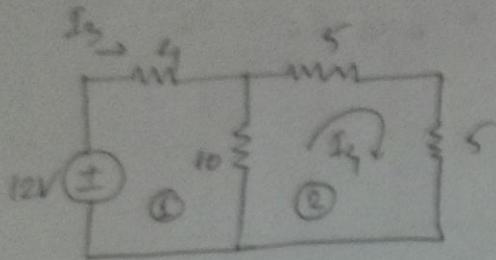

Applying KVL at mesh ①,

$$-12 + 4I_3 + 10(I_3 - I_4) = 0$$

$$\Rightarrow 14I_3 - 10I_4 = 12 \quad \text{--- (1)}$$

∴ From (1)

at mesh ②,

$$5I_4 + 5I_3 + 10(I_4 - I_3) = 0$$

$$\Rightarrow -10I_3 + 20I_4 = 0 \quad \text{--- (2)}$$

$$\therefore I_3 = \frac{4}{3} A \quad \text{and} \quad I_4 = \frac{2}{3} A$$

$$\therefore I_1 = I_1 + I_2 + I_3$$

$$= -\frac{5}{3} + \frac{-2}{3} + \frac{4}{3}$$

$$= -\frac{1}{3} A$$

$$= 0.111 A$$